



**Indian Institute of Technology Bombay**

**Analog Circuits Lab  
EE 230**

**Lab 5  
February 8, 2025**

**Mridul Choudhary  
23B3933**

# Contents

<b>1</b>	<b>Log and Anti-log Amplifier Hardware Implementation</b>	<b>2</b>
1.1	Aim of the experiment . . . . .	2
1.2	Procedure Outline . . . . .	2
1.3	Design of the circuit . . . . .	2
1.4	Experimental results . . . . .	4
1.5	Conclusion and Inference . . . . .	6
1.6	Experiment completion status . . . . .	7

# 1 Log and Anti-log Amplifier Hardware Implementation

## 1.1 Aim of the experiment

The experiment aims to design and implement an **analog square root computation circuit** using **logarithmic** and **anti-logarithmic amplifiers** based on operational amplifiers (op-amps). This builds upon the simulation performed in **Lab 4**, where the circuit behavior was verified using software tools. In this lab, the focus is on **hardware implementation** using real electronic components.

1. Implement a square root function using **log** and **anti-log amplifiers**.
2. Understand the **role of diodes** in logarithmic and exponential functions.
3. Explore **practical design considerations**, including component selection, diode characteristics, and circuit calibration.
4. Construct and test the circuit on a **breadboard** and verify the results experimentally.

## 1.2 Procedure Outline

### 1. Circuit Development:

- Use log-amp and anti-log amp configurations with diodes.
- Implement a four-block circuit with appropriate feedback resistors.
- Ensure proper bias voltage selection to eliminate offsets.

### 2. Hardware Implementation:

- Assemble the circuit on a breadboard using **TL084** op-amp.
- Use a multi-turn potentiometer for precision in setting bias voltages.
- Employ Keithley Digital Power Supply for controlled voltage input.

### 3. Testing & Analysis:

- Sweep  $V_{in}$  from 1V to 15V and record  $V_{out}$ .
- Compare experimental results with theoretical calculations.
- Plot  $V_{out}$  vs.  $V_{in}$  and  $\ln(V_{out})$  vs.  $\ln(V_{in})$  to validate circuit performance.
- Investigate the effects of diode polarity reversal and other component variations.

## 1.3 Design of the circuit

The circuit consists of four main blocks, each performing a specific function:

### 1. Block 1: Logarithmic Amplifier

- Converts the input voltage into a logarithmic form using a diode.
- Uses an inverting amplifier configuration to generate the log function.

### 2. Block 2: Offset Adjustment

- Eliminates offset voltage ( $a_2$  term in equations) using a reference voltage  $V_{b1}$ .
- Ensures that only the scaled logarithmic term is passed to the next stage.

### 3. Block 3: Scaling and Gain Adjustment

- Implements a scaling factor ( $\beta$ ) to achieve the required 1/2 exponent.
- The gain is set to ensure accurate scaling of the logarithmic term.

### 4. Block 4: Anti-Logarithmic Amplifier

- Converts the scaled log function back into an exponential (anti-log) output.
- Produces the final output  $V_{out} = \sqrt{V_{in}}$  using a second diode.

### 5. Additional Design Considerations:

- Choice of Diode:
  - Selected based on linearity in  $\ln(I_D)$  vs.  $V_D$  characteristics.
  - Should have minimal variation in saturation current ( $I_S$ ) and ideality factor ( $n$ ).
- Resistor and Bias Voltage Selection:
  - Values of  $R_3$ ,  $V_{b1}$ , and  $V_{b2}$  are tuned experimentally to achieve an accurate square-root response.
- Resistor  $R_3$  acts as a fine adjustment, while  $V_{b2}$  provides coarse tuning.

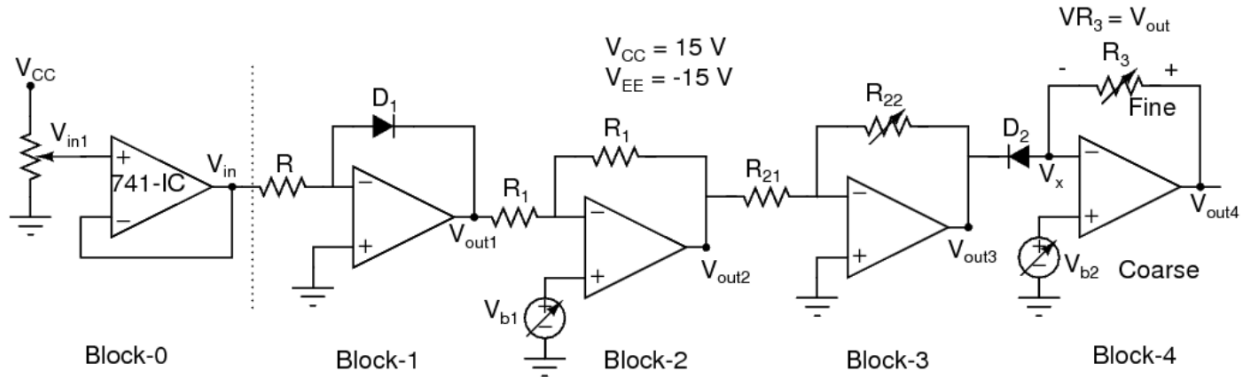


Figure 1: Square-Root Amplifier on Hardware

## 1.4 Experimental results

Sr. No.	Parameter	Value
1	$R_1$	10 k $\Omega$
2	$V_{b1}$	-0.178129838 V
4	$R_{21}$	10 k $\Omega$
5	$R_{22}$	Variable
6	$V_{b2}$	0.56 V
7	$R_3$	Variable
8	$V_{CC}$	15 V
9	$V_{EE}$	-15 V

Table 1: Various circuit parameters

Sr. No.	$V_{in}$	$V_{R_3}$
1	9.0 V	2.95 V
2	8.46 V	2.91 V
3	8.34 V	2.85 V
4	8 V	2.82 V
5	7.77 V	2.79 V
6	7 V	2.66 V
7	6.84 V	2.65 V

Table 2:  $V_{in}$  and  $V_{R_3}$  values

 


Figure 2: Circuit Diagram

 


Figure 3:  $V_{out}$  at  $V_{in}$  of 6.84 V

 


Figure 4:  $V_{out}$  at  $V_{in}$  of 8.46 V

## 1.5 Conclusion and Inference

### 1. What is the purpose of Block-0?

- Block-0 is likely a pre-conditioning stage that ensures a stable and well-defined input voltage before feeding it to the logarithmic amplifier. It could also provide buffering or level shifting.

### 2. What if $V_{in}$ is directly connected to $V_{in1}$ ?

- Directly connecting  $V_{in}$  to  $V_{in1}$  may bypass necessary impedance matching and cause errors in the log-amp response. The input voltage must be conditioned to ensure proper operation.

### 3. Determine the input impedance seen from $V_{in1}$ looking into the inverting terminal of Block-1.

- The input impedance is primarily determined by the resistor  $R$  used in the inverting amplifier configuration.

$$Z_{in} = R \quad (1)$$

### 4. Derive $V_{b1}$ and $V_{b2}$ DC voltages using a multi-turn potentiometer for better precision.

- $V_{b1}$  is set to cancel out the offset ( $a_2$  term in equation 12 in handout).
- $V_{b2}$  is adjusted to ensure correct scaling in the anti-log amplifier.

### 5. Tuning procedure for $V_{b1}$ , $V_{b2}$ , Block-3 Gain, and Resistor $R_3$ :

- Set  $V_{b1}$  by applying  $V_{in} = 1$  V and adjusting until the offset is removed.
- Adjust  $V_{b2}$  and  $R_3$  so that the voltage across  $R_3$  matches the square root function.
- Set the gain of Block-3 to ensure that  $b_2 = 1/2$ , maintaining the square root operation.

### 6. Tabulate the values of $V_{b1}$ and $V_{b2}$ .

- Already done in the previous section.

### 7. Why does the potentiometer in Block-4 act as a coarse adjustment, while $R_3$ is a fine adjustment?

- The potentiometer at the non-inverting terminal affects the overall offset, while  $R_3$  fine-tunes the gain.
- Mathematically:

$$V_{out} = R_3 I_{D2} + V_{b2} \quad (2)$$

- $V_{b2}$  affects the overall level (coarse adjustment).
- $R_3$  determines the sensitivity of the response (fine adjustment).

### 8. Tabulate $V_{in}$ vs. $V_{out}$ readings.

- Already done in the last section.
9. **Plot  $V_{out}$  vs.  $V_{in}$  for simulation, experimental, and theoretical results.**
    - Theoretical: Straight line (ideal behavior).
    - Experimental: Open circles (measured data).
    - Simulation: Cross symbols (SPICE results).
  10. **Plot  $\ln(V_{out})$  vs.  $\ln(V_{in})$  for simulation, experimental, and theoretical results.**
    - Ideal slope =  $1/2$ .
  11. **What should be the expected slope of  $\ln(V_{out})$  vs.  $\ln(V_{in})$  plot?**
    - Expected slope =  $1/2$ .
  12. **What happens if the polarity of diode  $D_2$  is reversed?**
    - The anti-log function will fail because the current flow direction is incorrect.
    - The exponential response will no longer be valid, causing an incorrect output.

This lab involves practical implementation of a square root amplifier using log and anti-log circuits with op-amps. The experiment builds upon previous simulations (Lab 4) and focuses on tuning the circuit for real-world accuracy. The results will be verified using both experimental and theoretical analysis, emphasizing circuit calibration and diode behavior.

## 1.6 Experiment completion status

The complete experiment was performed in front of the TA in the lab itself.