

Instructions:

- Write down all your observations in notebook.
- Verify your calculations with your respective TA.

1. Common Source (CS) Amplifier with Resistive Load

(a) Theory

i. Introduction:

MOSFET-based Common Source (CS) Amplifier with resistive load is as shown in the figure [1]. M_1 is an NMOS with R_D resistor as load. Input, V_{in} is applied at the gate of M_1 . V_{in} consists of DC bias voltage of V_{bias} and ac signal v_{in} (i.e. $V_{in} = V_{bias} + v_{in}$). V_{bias} is responsible for biasing M_1 in proper operating region. Output is observed at the drain of M_1 . This circuit is called a common source amplifier with a resistive load.

 


Figure 1: CS amplifier with Resistive Load

ii. Small signal gain (A_v):

Fig[2] is a small signal model of CS amplifier with resistive load. v_{in} is small signal applied between gate and source where source is grounded. This v_{in} causes change in current flowing from drain to source. This change is given by $g_m v_{in}$ where g_m is transconductance of M_1 mosfet. $g_m v_{in}$ flows from parallel combination of R_D and r_o (i.e. $R_D || r_o$) generating voltage change at drain (v_{out}) of $-g_m(R_D || r_o)v_{in}$. Thus, change of v_{in} voltage at gate causes $-g_m(R_D || r_o)v_{in}$ change in drain voltage. Gain (A_v) of CS amplifier is defined as v_{out}/v_{in} . Thus, $A_v = -g_m(R_D || r_o)$. For simplicity r_o is assumed infinite (Practically it is a high value). Thus small signal gain is simplified to $A_v = -g_m R_D$.

iii. Biasing M_1 in saturation region

M_1 should be biased in saturation region for amplifier to work. For this, $V_{ds1} > V_{gs1} - V_{th1}$. As a safety margin let us consider V_{ds1} is V_m voltage higher than $V_{gs1} - V_{th1}$. In our case $V_{ds1} = V_{out}$ and $V_{gs1} = V_{in} - V_{th}$. Let I_D be the current flowing through M_1 . Thus, V_{out} can be expressed as $V_{dd} - I_D R_D$. Thus the constraint to keep M_1 in saturation is $V_{dd} - I_D R_D = V_{in} - V_{th} + V_m$. I_D in saturation region is given as $\frac{K_n}{2}(V_{in} - V_{th})^2$ and transconductance, $g_m = K_n(V_{in} - V_{th})$. Thus $I_D R_D$ can be expressed as $\frac{A_v(V_{in} - V_{th})}{2}$. Substituting this in above inequality and rearranging terms to get V_{in} we get $V_{in} = \frac{V_{dd} - V_m}{1 + \frac{A_v}{2}} + V_{th}$. This V_{in} is the DC bias voltage (V_{bias}).

 


Figure 2: Small signal model of CS amplifier with resistive load

(b) **Experiment**

- Assemble CS amplifier on the breadboard. Apply $V_{dd} = 5V$. $V_{in} = 20mV_{pp}$, 1 KHz sinusoidal with V_{bias} DC offset. Use the value of V_{bias} and R_D as finalized after simulation.
- Tabulate the value of $V_{out_{dc}}$. Ensure M_1 is in the saturation region. If not then make the necessary changes. [1 Marks]
- Plot V_{out} and V_{in} on DSO. Set probe on AC mode. [2 Marks]
- Calculate small signal gain, A_v . If gain specifications are not met then make appropriate changes. [1 Marks]

2. Common Source (CS) Amplifier with Diode Connected Load

(a) **Theory**

i. **Introduction**

 


Figure 3: CS amplifier with diode connected load

ii. **Small signal gain (A_v)**

Small signal model of CS amplifier with diode connected load is shown in Fig.[4]. For simplicity let us consider r_{o1} and r_{o2} be infinite (In practical cases both these resistances are very high but not infinite). Thus there is no current flowing through these resistances. Writing KCL at node v_{out} we get $g_{m2}v_{sg2} = g_{m1}v_{gs1}$. Where $v_{gs1} = v_{in}$ and $v_{sg2} = -v_{out}$. g_{m1} can be expressed as $\sqrt{2I_{d1}K_{n1}}$ similarly g_{m2} can be expressed as $\sqrt{2I_{d2}K_{p2}}$. Thus $A_v = \frac{v_{out}}{v_{in}} = \frac{-g_{m1}}{g_{m2}} = -\sqrt{\frac{K_{n1}}{K_{p1}}}$

iii. **Biasing M_1 , M_2 in saturation region**

Drain and Gate of M_2 are connected to each other. Thus M_2 if on then will always be biased in saturation region. M_1 will remain in saturation as long as $V_{out} > V_{in} - V_{th1}$. Thus, $V_{out} = V_{in} -$

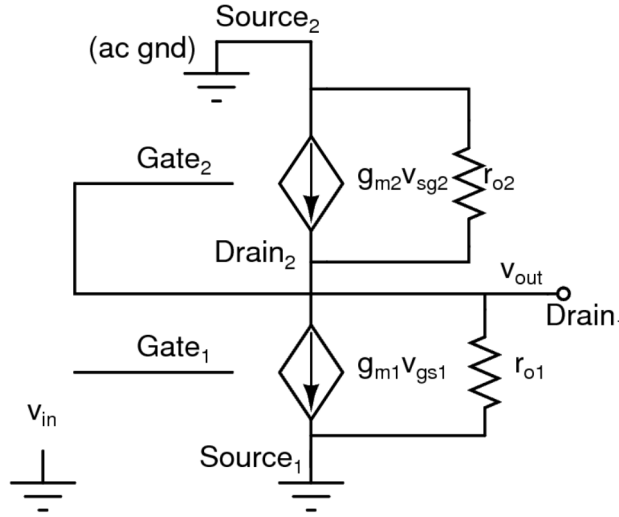


Figure 4: Small signal model of CS amplifier with diode connected load

$V_{th1} + V_m$. Current from M_2 and M_1 are same. Thus, $K_{n1}(V_{in} - V_{th1})^2 = K_{p2}(V_{dd} - V_{out} - V_{th2})^2$. Input voltage can be expressed as $V_{in} = \sqrt{\frac{K_{p2}}{K_{n1}}}(V_{dd} - V_{out} - V_{th2}) + V_{th1}$. Let V_m be the margin voltage by which V_{out} is greater than $V_{in} - V_{th1}$. Substituting this in V_{in} equation we can solve for V_{in} . This value will be the bias voltage (V_{bias}) of M_1 .

(b) **Experiment**

- Assemble CS amplifier with diode connected load on the breadboard. Apply $V_{dd} = 5V$. $V_{in} = 20mV_{pp}$, 1 KHz sinusoidal with V_{bias} DC offset. Use the value of V_{bias} as finalized after simulation. [1 Marks]
- Tabulate the value of $V_{out_{dc}}$. Ensure M_1 is in the saturation region. If not then make the necessary changes. [2 Marks]
- Plot V_{out} and V_{in} on DSO. Set the probe on AC mode. [1 Marks]
- Calculate small signal gain, A_v . Compare results with the hand-calculated and simulated results. [1 Marks]

3. Current Mirror (CM) Design

(a) **Introduction**

Current mirror is an analog circuit which senses the reference current and mirrors it to the load. It is widely used in modern ICs. Most common applications are amplifiers, D/A converters, Delay elements, Bias circuits etc.

(b) **Basic Design Concepts**

Basic idea is to generate a reference voltage (V_{GS1}) by pushing current (I_{REF}) into the diode connected MOSFET (M_1) as shown in Fig.[5] and use this voltage to bias another MOSFET (M_2) such that the another MOSFET acts as a current source providing same current (I_{copy}) as reference current (I_{REF}). Let's derive the equation for I_{COPY} in terms of I_{REF} and device parameters.

The current equation of a MOSFET, ignoring channel length modulation and biased in saturation region is

$$I_{DS} = \frac{1}{2} \mu C_{OX} \frac{W}{L} (V_{GS} - V_{TH})^2 \quad (1)$$

Above equation can be rearranged to get

$$V_{GS} = \sqrt{\frac{2I_{ds}}{\mu C_{OX} \frac{W}{L}}} + V_{TH} \quad (2)$$

Referring to Fig.[5] and Eqn.[2] we can write V_{GS1} as

$$V_{GS1} - V_{TH1} = \sqrt{\frac{2I_{REF}}{\mu C_{OX} \frac{W_1}{L_1}}} \quad (3)$$

Since $V_{GS1} = V_{GS2}$ and assuming $V_{TH1} = V_{TH2}$ we can write I_{COPY} as

$$I_{COPY} = \frac{1}{2} \mu C_{OX} \frac{W_2}{L_2} (V_{GS1} - V_{TH1})^2 \quad (4)$$

$$I_{COPY} = \frac{W_2}{L_2} \frac{I_{REF}}{\frac{W_1}{L_1}} \quad (5)$$

generally written as

$$\frac{I_{COPY}}{\frac{W_2}{L_2}} = \frac{I_{REF}}{\frac{W_1}{L_1}} \quad (6)$$

In many applications we may require to copy more current from reference. This is simply achieved by connecting current source MOSFETs in parallel and with appropriate sizing.

Note that all the above equations are derived by ignoring channel length modulation effect thus if this effect is considered there may be error in copying current, usually length of devices are chosen high to minimize the error and V_{DS1} , V_{DS2} are made equal. Both the MOSFETs (M1 and M2) are in saturation region. Since, M1 is in diode connected it will always be in saturation region given enough overdrive is provided but there is a possibility of M2 going in triode region due to inadequate drain to source voltage across it. Thus, if M2 is biased in triode then current mirroring will not happen. The derived equation is valid for older technology models where MOSFET obeys the square law behaviour. In small scale devices this is not true but however it will still be able to mirror the current but will follow different equation as opposed to Eqn.[6]

 


Figure 5: Basic NMOS current mirror circuit

(c) Experiment

- i. Fig.[8] shows a basic current mirror to be implemented on the breadboard. R1 is a fixed resistor, designed to achieve desired $I_{REF} = 2mA$. A1 and A2 are Ammeters used to measure current I_{REF} and I_{COPY} respectively. R2 is a potentiometer used to vary the load of M_2 .
- ii. Draw a PMOS equivalent basic current mirror. [2 Marks]
- iii. Use the value of R1 as derived from the simulation. VDD = 8 V. Measure I_{REF} . Compare with the simulation result. [2 Marks]
- iv. Now sweep V_{DS2} from 0 V to 8 V in 500 mV step size (include the value of V_{DS1}). This can be achieved by sweeping the potentiometer R2 appropriately. Measure the readings of I_{REF} , I_{COPY} , V_{DS1} and V_{DS2} . [2 Marks]
- v. When is the error between I_{COPY} and I_{REF} minimum? [1 Marks]
- vi. What changes are required to design the current mirror for $I_{COPY} = N \cdot I_{REF}$. Where N is a positive integer. [1 Marks]
- vii. Draw the modified circuit in the notebook when $N = 2$ ($I_{COPY} = N \cdot I_{REF}$) [2 Marks]

 


Figure 6: Basic NMOS current mirror circuit

 


Figure 7: CD4007 Pinout Circuit

 


Figure 8: CD4007 IC Diagram