

END SEMESTER EXAM SOLUTION

EE 230

Maximum Marks

43



Section - I

Working of the circuit

(2.5 M)

I.D. (i). As $V_{trig} < LTP$, R become 1 (SR LATCH Resets)

(ii). Q becomes 0 and Q_1 (BJT) turns OFF
 \bar{Q} becomes 1 which is V_{out}

(iii). Now C_1 (Capacitor) charges.

(iv). This will continue until $V_Q \geq UTP$

$$\text{Now } S = 1$$

$$R = 0$$

(v). Now for this $\bar{Q} = 0 = V_{out}$

$Q = 1$ which turns on Q_1 (BJT)
and C_1 dis-charges

(vi). Now $S = 0, R = 0$ so Q & \bar{Q} latches to 1, 0
respectively

(vii) $V_{out} = 0$ which is the stable state of V_{out} .


Maximum Value of Trigger Voltage

$$V_{LTP} = \frac{1}{3} V_{ce} = 3 \text{ Volts} \quad (1 \text{ M})$$

Output waveforms (waveforms for derivation)

1.2).

V_{out}

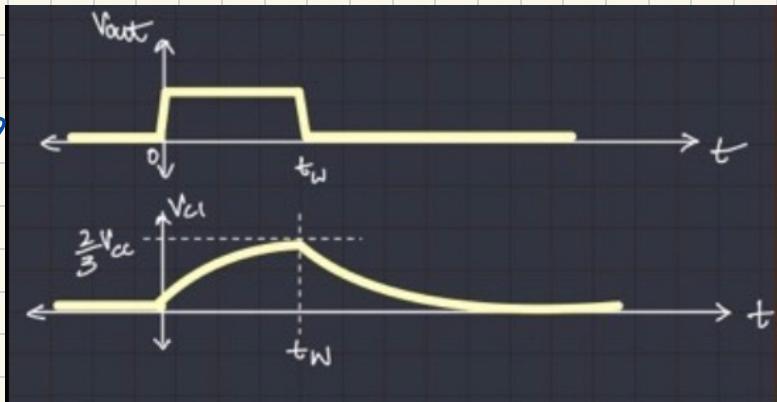

optional

derivation

Equation of 1st order RC circuit:

$$V_C(t) = V_{cc} (1 - e^{-t/\tau}); \tau = R_1 \cdot C_1$$

$$\frac{2}{3} V_{cc} = V_{cc} (1 - e^{-t_w/\tau})$$

$$e^{-t_w/\tau} = \frac{1}{3}$$

$$t_w = \ln 3 \cdot \tau = 1.1 R_1 C_1$$

2.5M

pulse width depends upon circuit parameters

1.3). Table filling

Inputting Time	V_{trig}	S R	\bar{Q} $\bar{\bar{Q}}$	BJT(Q_1) (ON/OFF)	V_{C1} (Charging or Discharging)	V_{C1} (Voltage)
0	V_{cc}	0 0	1 0	ON	Discharge	$0 \rightarrow R_1$
0^+	0	0 1	0 1	OFF	charge	$0 \rightarrow R_2$
t_w	V_{cc}	0 0	0 1	OFF	charge	$>0 \rightarrow R_3$
t_w^+	V_{cc}	1 0	1 0	ON	discharge	$\frac{2}{3} V_{cc} \rightarrow R_4$
$>t_w$	V_{cc}	0 0	1 0	ON	discharge	$<\frac{2}{3} V_{cc} \rightarrow R_5$

Each row carries 0.6M

$$0.6 \times 5 = 3M$$

Section-2

Q-1) PWM generates


$$PW_{\min} \approx 1.5 - 2 \text{ ms} \quad (1.25 \text{ ms})$$

$$PW_{\max} \approx 3 - 4 \text{ ms} \quad (1.25 \text{ ms})$$

Showing the o/p to TA $\rightarrow (1.5 \text{ ms})$

<just check for Max and Min pulse width>

Example

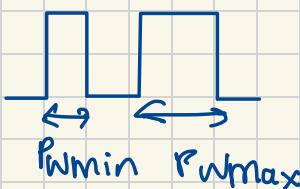

Q-2) derivation of Maximum & Minimum pulse width.

for PWM the circuit is same as monostable with UTP with extra signal added with DC

$$\text{so } V_{c_1}(t) = V_{cc} (1 - e^{-t/\tau}) = \text{UTP}$$

$$e^{-t/\tau} = 1 - \frac{\text{UTP}}{V_{cc}}$$

$$= 1 - \left(\frac{\frac{2}{3} V_{DD} + V_m(t)}{V_{cc}} \right)$$

$$e^{-t/\tau} = \frac{1}{3} + \left(\frac{V_m(t)}{V_{cc}} \right)$$

$$t_p = -\tau \ln \left(\frac{1}{3} + \frac{V_m(t)}{V_{cc}} \right)$$

LM

If $V_m(t) = A \sin \omega t$


$$\text{So Width max} = -\tau \ln \left(\frac{1}{3} - \frac{A}{V_{cc}} \right) \quad (0.5 \text{ ms}) \quad \tau = 2.2 \text{ ms}$$

$$\text{Width min} = -\tau \ln \left(\frac{1}{3} + \frac{A}{V_{cc}} \right) \quad (0.5 \text{ ms}) \quad W_{\max} = 3.3 \text{ ms} \quad W_{\min} = 1.78 \text{ ms}$$

These will include discuss & compare Part.

Astable Timer Circuit

2.3).

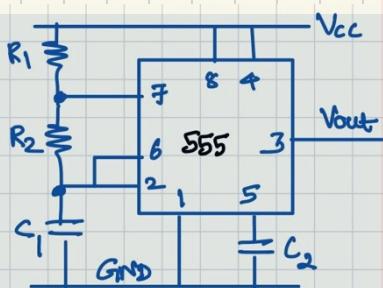


Initial conditions

$$Q=0, \bar{Q}=1$$

\downarrow pin 3

goes to ESR
Base

0.5M

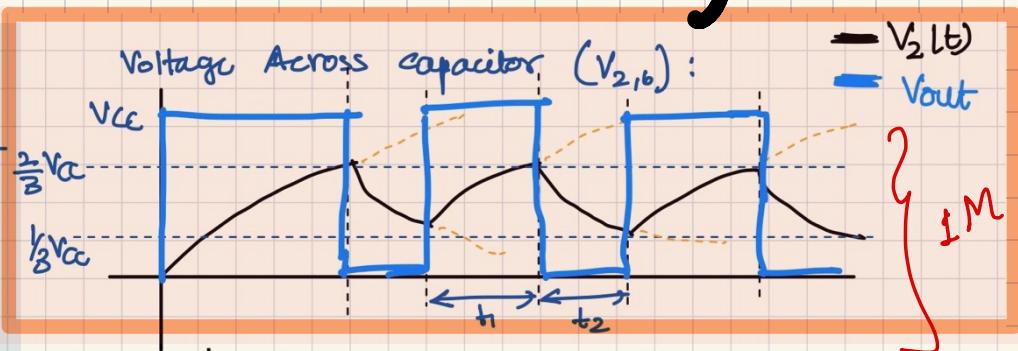

- 1) From $\frac{1}{3}V_{CC}$ it charges <just skip on cycle> till $\frac{2}{3}V_{CC}$ by the path



$$V_2(t) = V_{final} + (V_{int} - V_{final}) e^{-t/\tau_1}$$

$$\text{Where } \tau_1 = (R_1 + R_2) C_1$$

$$V_{final} = V_{CC}$$

$$V_{int} = \frac{1}{3} V_{CC}$$

$$V_2(t) = V_{CC} - \frac{2}{3} V_{CC} e^{-t/\tau_1}$$


$$V_2(t_1) = V_{CC} - \frac{2}{3} V_{CC} e^{-t_1/\tau_1} = \frac{2}{3} V_{CC}$$

$$\Rightarrow \frac{2}{3} V_{CC} e^{-t_1/\tau_1} = \frac{1}{3} V_{CC}$$

$$\Rightarrow t_1 = \ln 2 \cdot (R_1 + R_2) C_1$$

- 2). From $\frac{2}{3}V_{CC}$ it discharges

till $\frac{1}{3}V_{CC}$ by the path

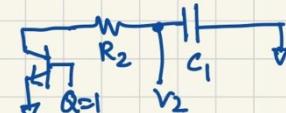

$$V_2(t) = V_{final} + (V_{int} - V_{final}) e^{-t/\tau_2}$$

$$\text{Where } \tau_2 = R_2 C_1$$

$$V_{final} = 0$$

$$V_{int} = \frac{1}{3} V_{CC}$$

$$\therefore V_2(t) = \frac{2}{3} V_{CC} e^{-t/\tau_2}$$

$$\text{At } t_2 \Rightarrow V_2(t_2) = \frac{2}{3} V_{CC} e^{-t_2/\tau_2} = \frac{1}{3} V_{CC}$$

$$\Rightarrow t_2 = \ln 2 \cdot R_2 C_1$$

$$\text{Time period} = t_1 + t_2 = \ln 2 \cdot (R_1 + 2R_2) \cdot C_1 = 0.693 (R_1 + 2R_2) \cdot C_1$$


$$f_{out} = \frac{1.44}{(R_1 + 2R_2) \cdot C_1}$$

Section → 3 → IC Testing (JM)

4.1).

2).

a).

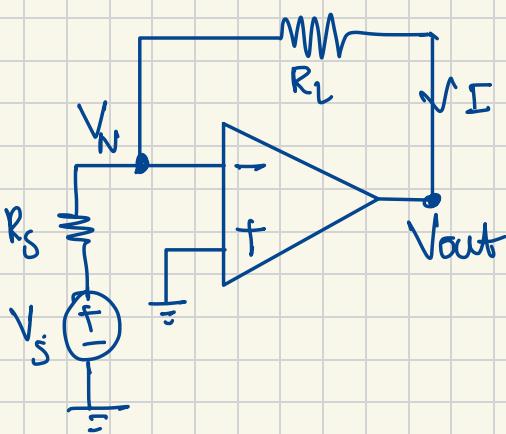

$$\left. \begin{aligned} I &= \frac{V_s - V_N}{R_s} \\ I &= \frac{V_N - V_{out}}{R_L} \end{aligned} \right\}$$

By Virtual Ground

$$I = \frac{V_s}{R_s} = -\frac{V_{out}}{R_L}$$

$$I = \frac{V_s}{R_s}$$

JM

clearly I depends on V_s , R_s and V_{out}

will vary according to R_L to leave Constant
current until the op-Amp saturates

JM

2).
b).

$$|Gain| = \left| \frac{V_{out}}{V_{in}} \right| = \frac{R_L}{R_s}$$

For the op-Amp not to be in } $|V_{out}| < V_{SAT}$
saturation }

$$\frac{R_L}{R_s} \times |V_{in}| < V_{SAT}$$

$$R_L < \frac{V_{SAT} \times R_s}{|V_{in}|} = \frac{15 \times 10k}{5}$$


$$R_L < 30k\Omega$$

$$I(R_L) = \begin{cases} \frac{V_s}{R_s} & \text{for } R_L < 30k\Omega \\ \frac{V_s + V_{SAT}}{R_s + R_L} & \text{for } R_L \geq 30k\Omega \end{cases}$$

0.5 M

$$R_s = 10k\Omega$$

$$V_s = 5V$$

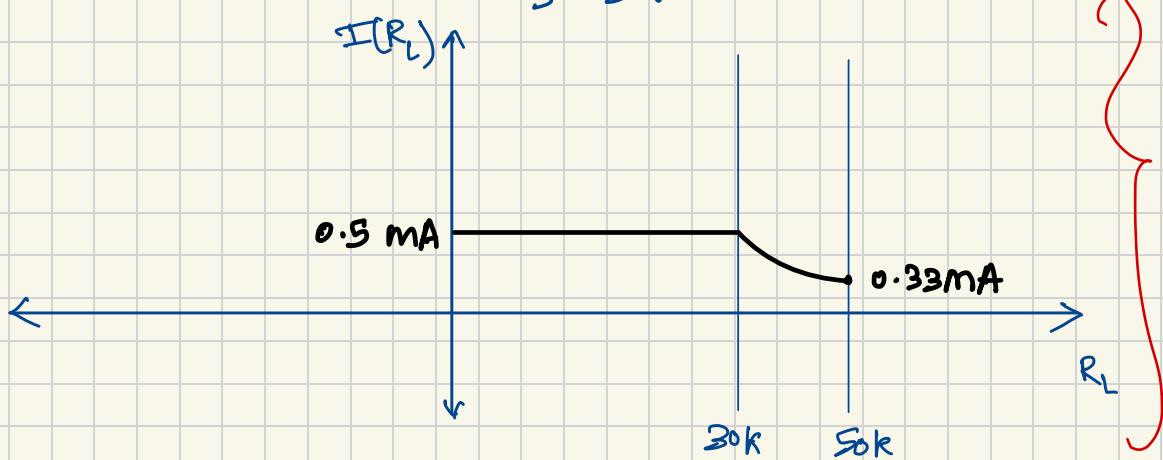


(c) Bread Board Implementation (2M)
↳ Reporting R_L Value

Hardware

4.2).

a).

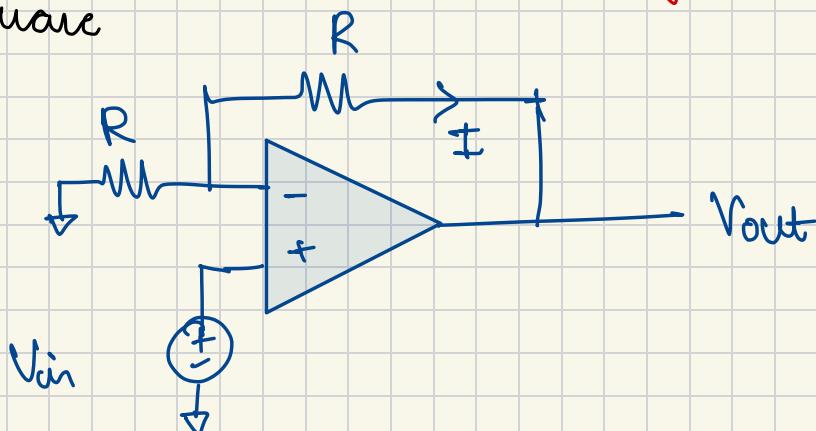


$$(b). \quad I = 0.5mA$$


$$\frac{V_{out}}{V_{in}} = 1 + \frac{R}{M} = 2$$

3M

c).

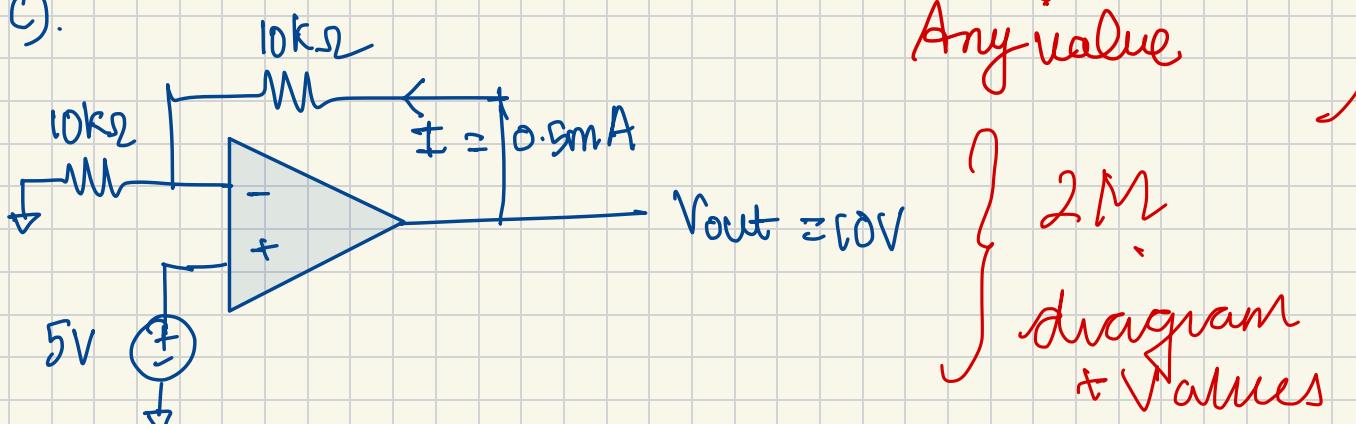

d) Showing Result to TA ! - gain = 2 2M

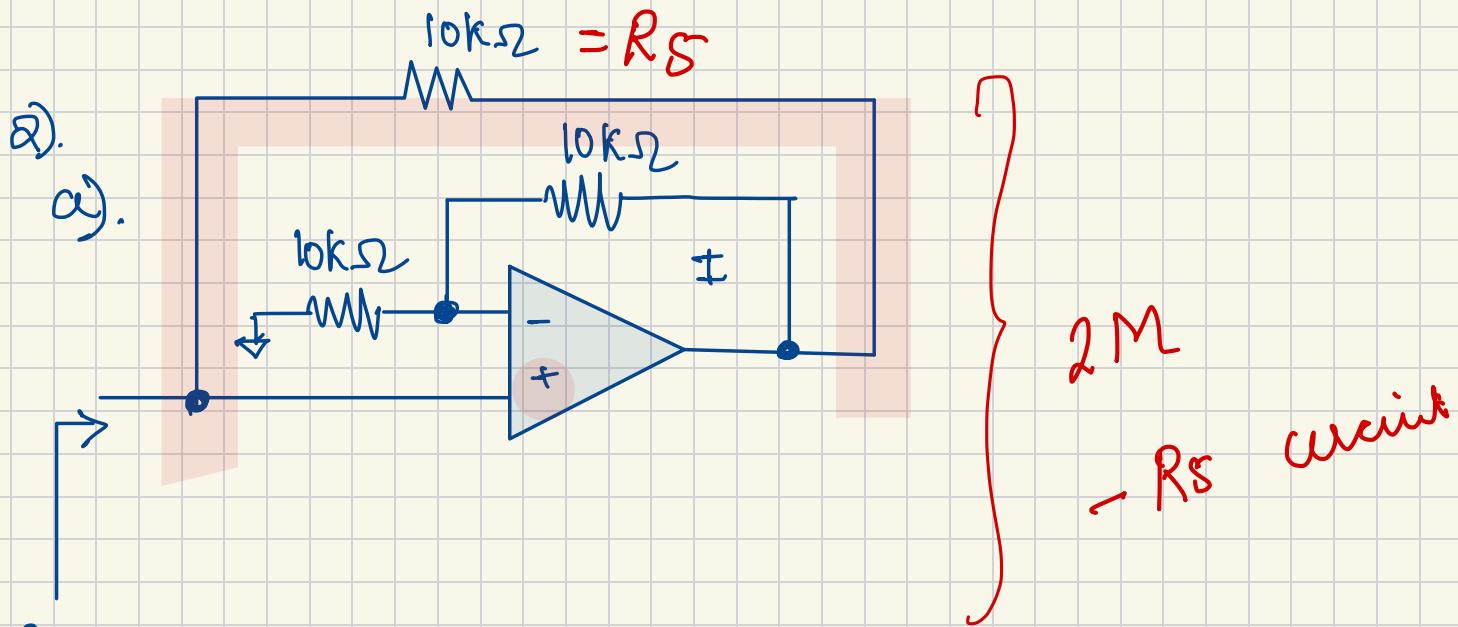



b)

$$V_x = \frac{V_s}{2}$$


$$I = \frac{V_s}{2R_s}$$

E Breadboard Implementation

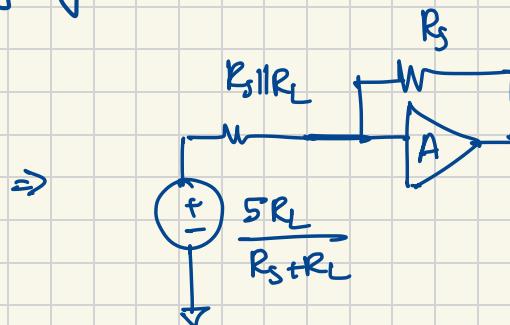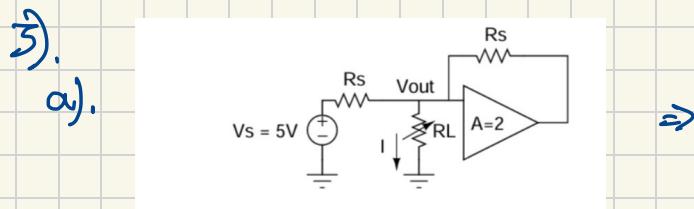→ Verifying the current (TA) $\rightarrow 2\text{ M}$



Since $V_{cc} = \pm 15\text{ V}$

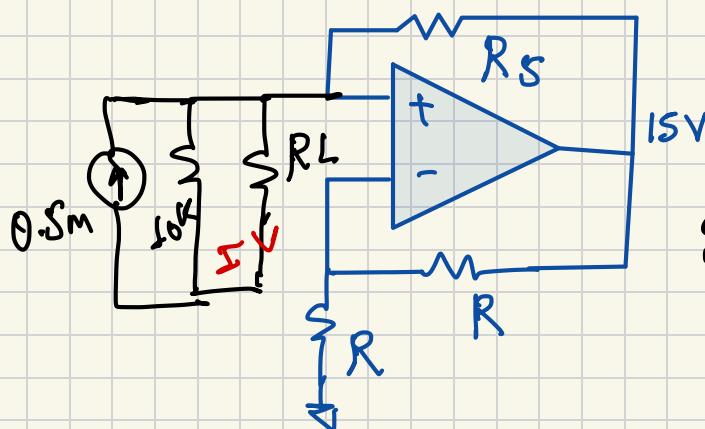


$$V_- \Rightarrow \frac{15}{2} = 7.5\text{ V}$$

$$V_- = V_+ = 7.5\text{ V}$$

$$\text{So } I = \text{constant} = \frac{V}{R_L}$$
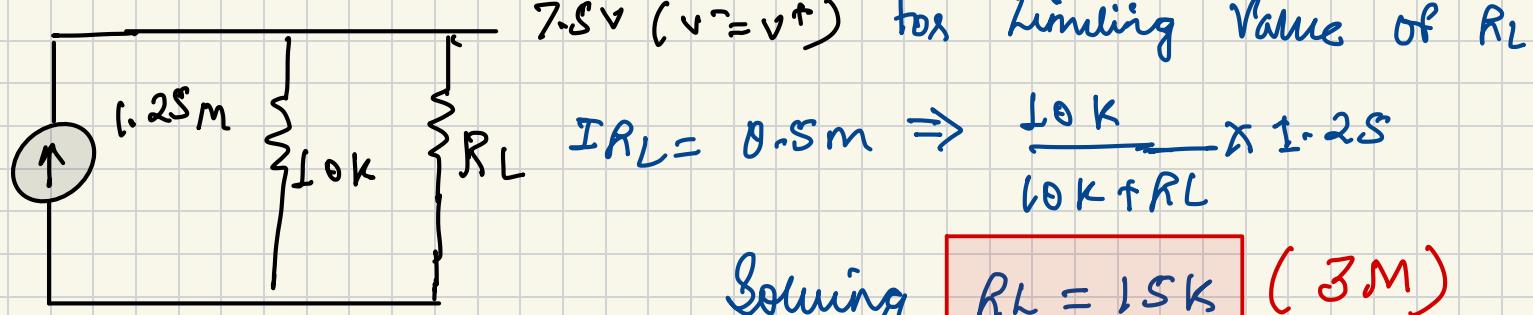
$$I_{10\text{k}} = \frac{7.5}{10} = 0.75\text{ mA}$$



7.5V ($v^- = v^+$) For Limiting Value of R_L

$$I_{RL} = 0.5 \text{mA} \Rightarrow \frac{10 \text{k}}{10 \text{k} + R_L} \times 1.25$$

Solving $R_L = 15 \text{k}$ (3M)