

1. Wien Bridge Oscillator

(a)	Frequency	Magnitude	phase
	100 Hz	880 mV _{pp}	74.66°
	500 Hz	2.8 V _{pp}	29.16°
	1000 Hz	3.28 V _{pp}	3.84°
	2000 Hz	2.96 V _{pp}	-18.91°
	3000 Hz	2.56 V _{pp}	-35.76°
	4000 Hz	2.16 V _{pp}	-48.46°
	5000 Hz	1.84 V _{pp}	-51.36°
	10 kHz	1.04 V _{pp}	-70.44°
	30 kHz	400 mV _{pp}	-61.44°
	20 kHz	600 mV _{pp}	-78.05°

Cutoff is near 1K Hz, hence we are taking more measurements \Rightarrow

\Rightarrow	1.1 kHz	3.2 V _{pp}	316 mdeg
	1.2 kHz	3.2 V _{pp}	-4.5°
	1.03 kHz	3.2 V _{pp}	0 deg

At the cut-off frequency, the output voltage is maximum and the phase difference b/w the input and output is 0.

(b) Resonance Condition $\Rightarrow f_0 = \frac{1}{2\pi RC}$ will have phase

difference of 0°.

Oscillations \Rightarrow If loop gain $AB = 1$ then the circuit sustains oscillation.

$$(c) \text{ Cutoff frequency} = \frac{1}{2\pi RC} = 1.59 \text{ kHz}$$

$$R = 10 \text{ k}\Omega \quad C = 10 \text{ nF}$$

(d)

$$\text{Measured frequency} = 1.174 \text{ kHz}$$

$$V_{pp} = 21 \text{ V}$$

$$(e) \text{ at } R_1 = R_2 = 5 \text{ kHz}$$

$$\text{Measured frequency} = 2.4 \text{ kHz}$$

$$V_{pp} = 21.2 \text{ V}$$

2. Sallen - Key Active Low-pass Filter

$$F_c * FSF = \frac{1}{2\pi RC \sqrt{m}}$$

frequency scaling factor

$$\text{Quality factor } Q = \frac{\sqrt{m}}{m+1}$$

$$F_c = 1 \text{ kHz}$$

1V_{pp} input

(a) Butterworth $R_2 = 18.4 \text{ K}\Omega$ $C_1 = 0.01 \mu\text{F}$

$$R_1 = mR_2 \quad C_2 = nC_1$$

$$FSF = 1 \quad Q = \frac{1}{\sqrt{2}} \quad f_c = 1 \text{ KHz}$$

$$10^3 \times 1 = \frac{1}{\sqrt{2}} \quad \text{--- (1)}$$

$$2 \times \pi \times 18.4 \times 10^3 \times 10 \times 10^{-9} \sqrt{mn}$$

$$\frac{1}{\sqrt{2}} = \frac{\sqrt{mn}}{m+1} \quad \text{--- (2)}$$

from (1) $\sqrt{mn} = 0.8649$

from (2) $m+1 = \sqrt{2} (0.8649) \Rightarrow m = 0.22325$
 $n = 3.3506$

$$R_1 = 4.1078 \text{ K} \quad C_2 = nC_1 = 33.5 \text{ nF}$$

frequency	magnitude	frequency	magnitude
10 Hz	1.048 V _{pp}	150 Hz	1.016 V _{pp}
50 Hz	1.048 V _{pp}	200 Hz	992 V _{pp}
100 Hz	1.04 V _{pp}	250 Hz	968 V _{pp}
500 Hz	856 mV _{pp}	300 Hz	960 V _{pp}
1000 Hz	536 mV _{pp}	350 Hz	928 V _{pp}
1.5 KHz	440 mV _{pp}	400 Hz	936 V _{pp}
2 KHz	272 mV _{pp}	450 Hz	904 V _{pp}
2.5 KHz	168 mV _{pp}		
3 KHz	112 mV _{pp}		
3.5 KHz	72 mV _{pp}		
4 KHz	96 mV _{pp}		
5 KHz	72 mV _{pp}		
7.5 KHz	48 mV _{pp}		
10 KHz	40 mV _{pp}		

b) Chebyshev $R_2 = 7.32 \text{ k}\Omega$ $C_1 = 0.014 \text{ F}$

$$FSF = 0.8414 \quad Q = 1.3049$$

$$10^3 \times 0.8414 = \frac{1}{2\pi \times 7.32 \times 10^3 \times 10 \times 10^{-9} \times \sqrt{m}}$$

$$1.3049 = \frac{\sqrt{m}}{m+1}$$

from ① $\sqrt{m} = 2.584$

from ② $m+1 = \frac{2.584}{1.3049} \Rightarrow m = 0.98022$

$$\Rightarrow n = 6.8177$$

$$\Rightarrow R_1 = 7.175 \times 10^3 \Omega$$

$$C_2 = 68.177 \text{ nF}$$

$$R_2 = 7.32 \text{ k}\Omega$$

$$C_1 = 10 \text{ nF}$$

frequency

magnitude

50 Hz

1.016V

100 Hz

1.024V

150 Hz

1.040V

200 Hz

1.054V

250 Hz

1.088V

300 Hz

1.112V

350 Hz

1.144V

400 Hz

1.184V

450 Hz

1.216V

500 Hz

1.256V

1000 Hz

0.704V

600 Hz

1.280V

700 Hz

1.200V

800 Hz

1.048V

900 Hz

0.864V

1500 Hz

0.304V

2000 Hz

0.160V

3000 Hz

0.080V

3500 Hz

0.056V

5000 Hz

0.032V

7500 Hz

0.016V

10K Hz

0.008V

3. Multiple - feedback active band-pass filter

(a) $R_1 = 68 \text{ k}\Omega$ $R_2 = 180 \text{ k}\Omega$ $R_3 = 2.7 \text{ k}\Omega$
 $C_1 = C_2 = 0.01 \text{ }\mu\text{F}$

(b) $F_0 = \frac{1}{2\pi C} \sqrt{\frac{R_1 + R_3}{R_1 R_2 R_3}}$ $C = C_1 = C_2$

Bandwidth $= \frac{F_0}{Q}$ $Q = \pi F_0 C R_2$

$$F_0 = \frac{1}{2 \times \pi \times 10^{-8} \times} \sqrt{\frac{(68 + 2.7) \times 10^3}{68 \times 10^3 \times 2.7 \times 10^3 \times 180 \times 10^3}}$$

$$= 736.135 \text{ Hz}$$

Bandwidth $= \frac{F_0}{Q} = \frac{1}{\pi R_2 C} = 176.9285 \text{ Hz}$

frequency	magnitude
50 Hz	80 mVpp
100 Hz	100 mVpp
150 Hz	152 mVpp
200 Hz	208 mVpp
250 Hz	240 mVpp
300 Hz	312 mVpp
350 Hz	400 mVpp
400 Hz	576 mVpp
450 Hz	800 mVpp

500 Hz	1.088 V
1000 Hz	896 mVpp
600 Hz	896 mVpp
700 Hz	568 mVpp
800 Hz	400 mVpp
900 Hz	328 mVpp
1000 Hz	272 mVpp
1500 Hz	160 mVpp
2000 Hz	104 mVpp
2500 Hz	96 mVpp
3000 Hz	80 mVpp
3500 Hz	64 mVpp
5000 Hz	56 mVpp
7500 Hz	40 mVpp
10 K Hz	40 mVpp

Nauman
21/2/25