



Indian Institute of Technology Bombay

Analog Circuits Lab
EE 230

Lab 4
February 4, 2025

Mridul Choudhary
23B3933

Contents

1	Log and Anti-Log Amplifier	2
1.1	Aim of the experiment	2
1.2	Design of the Circuit	2
1.3	Experimental Results	3
1.4	Conclusion and Inference	6
1.5	Experiment Completion Status	7

1 Log and Anti-Log Amplifier

1.1 Aim of the experiment

1. **Understand and Implement Log and Anti-Log Amplifiers:** Design and analyze circuits that compute the logarithm and antilogarithm of an input signal.
2. **Develop a Square Root Amplifier:** Use logarithm and antilogarithm principles to construct a circuit that outputs the square root of the input voltage.
3. **Analyze the Behavior of Diodes in Logarithmic and Antilogarithmic Circuits:** Study the diode's voltage-current characteristics and its role in logarithmic computations.
4. **Simulate the Square Root Amplifier Circuit:** Validate circuit performance through SPICE simulations, comparing theoretical and simulated results.

1.2 Design of the Circuit

The experiment uses op-amps and diodes to implement logarithmic, anti-logarithmic, and square root functions.

1. Logarithmic Amplifier Design

- Uses a diode and an op-amp in an inverting amplifier configuration.
- Key Equation:

$$I_D = I_s(e^{\frac{V_D}{nV_T}} - 1) \quad (1)$$

- If $V_D \gg nV_T$, approximation holds :

$$I_D = I_s e^{\frac{V_D}{nV_T}} \quad (2)$$

- Applying to the circuit:

$$I_D = \frac{V_{in}}{R} \quad (3)$$

- Resulting in:

$$V_{out1} = -nV_T \ln(V_{in}) + a_2 \quad (4)$$

- This circuit transforms input voltage into a logarithmic signal.

2. Offset Removal Block

- A subtraction circuit removes the offset term a_2 .
- After subtraction:

$$V_{out2} = a_1 \ln(V_{in}) \quad (5)$$

3. Scaling Block

- The log output is scaled by $1/2$ using an amplifier with gain $\beta = \frac{1}{2}$

- Output:

$$V_{out3} = \frac{-a_1}{2} \ln(V_{in}) \quad (6)$$

4. Antilogarithmic Amplifier

- Uses a second diode to exponentiate the scaled output.
- Applying the exponential equation:

$$V_{out} = R_3 I_s e^{\frac{V_{b2}}{n_2 V_T}} V_{in}^{\frac{1}{2}} + V_{b2} \quad (7)$$

- Final square-root result:

$$V_{out} = b_1 V_{in}^{\frac{1}{2}} \quad (8)$$

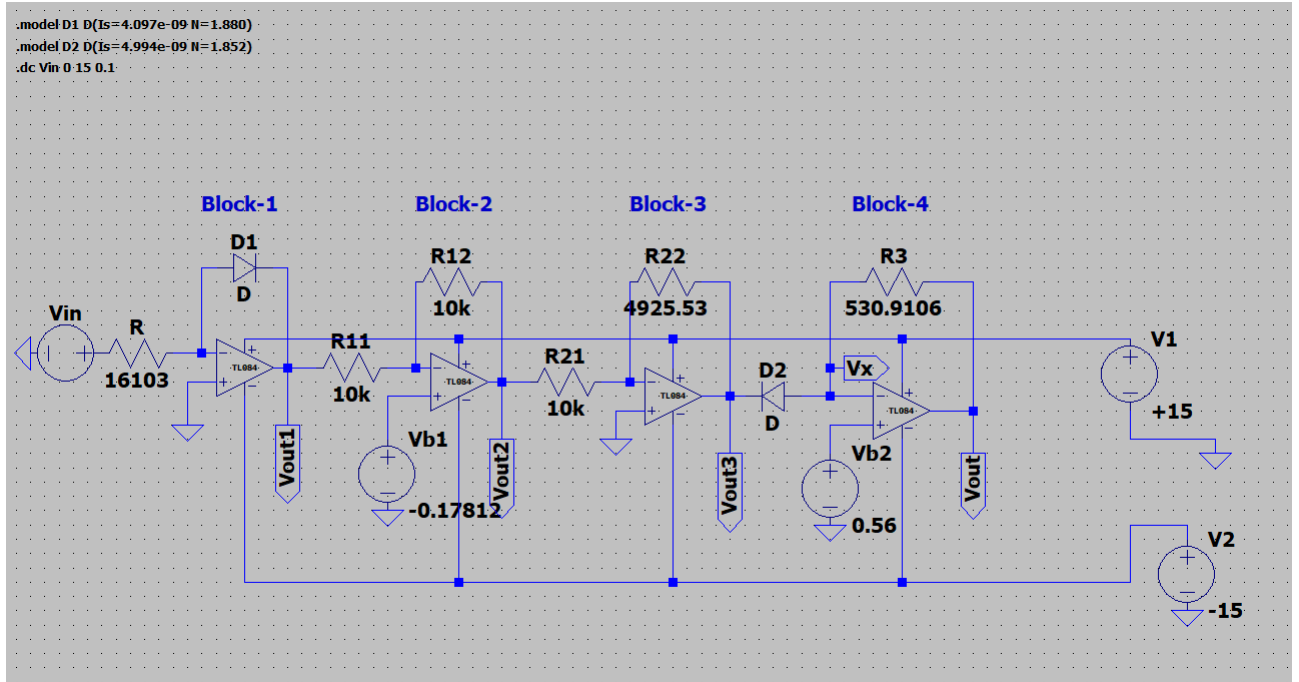


Figure 1: Log Anti-Log Circuit Diagram

1.3 Experimental Results

Sr. No.	Parameter	Value
1	n_1	1.880
2	n_2	1.852
3	I_{s1}	$4.097e^{-09}$ A
4	I_{s2}	$4.994e^{-09}$ A
5	(V_{d1}, I_{d1}) (D1)	(0.5 V, $1.192e^{-04}$ A)

6	(V_{d2}, I_{d2}) (D1)	$(0.6 \text{ V}, 9.315e^{-04} \text{ A})$
7	(V_{d1}, I_{d1}) (D2)	$(0.5 \text{ V}, 1.698e^{-04} \text{ A})$
8	(V_{d2}, I_{d2}) (D2)	$(0.6 \text{ V}, 1.368e^{-03} \text{ A})$
9	R	16103Ω
10	a_1	0.048645
11	a_2	-0.35625967791100094
12	R_1	$10 \text{ k}\Omega$
13	V_{b1}	-0.178129838 V
14	β	0.492553
15	R_{21}	$10 \text{ k}\Omega$
16	R_{22}	4925.53Ω
17	V_{b2}	0.56 V
18	R_3	530.9106Ω

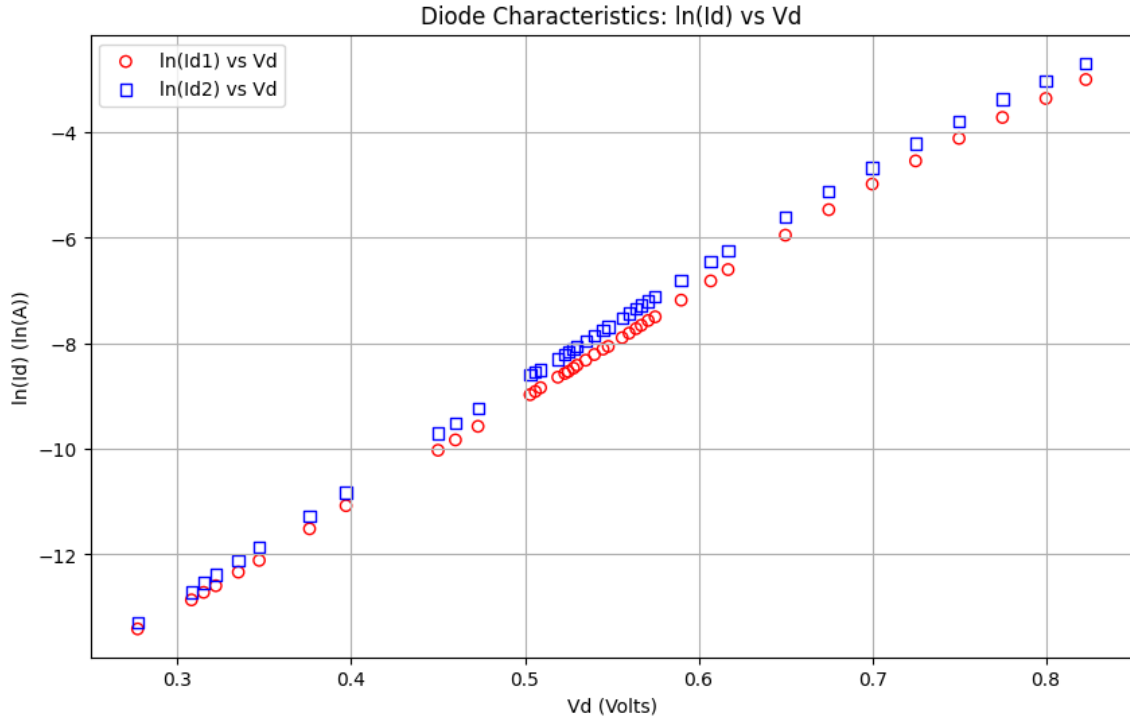


Figure 2: V_D v/s I_D of D1 and D2

 


Figure 3: Fitted line on V_D v/s I_D of D1

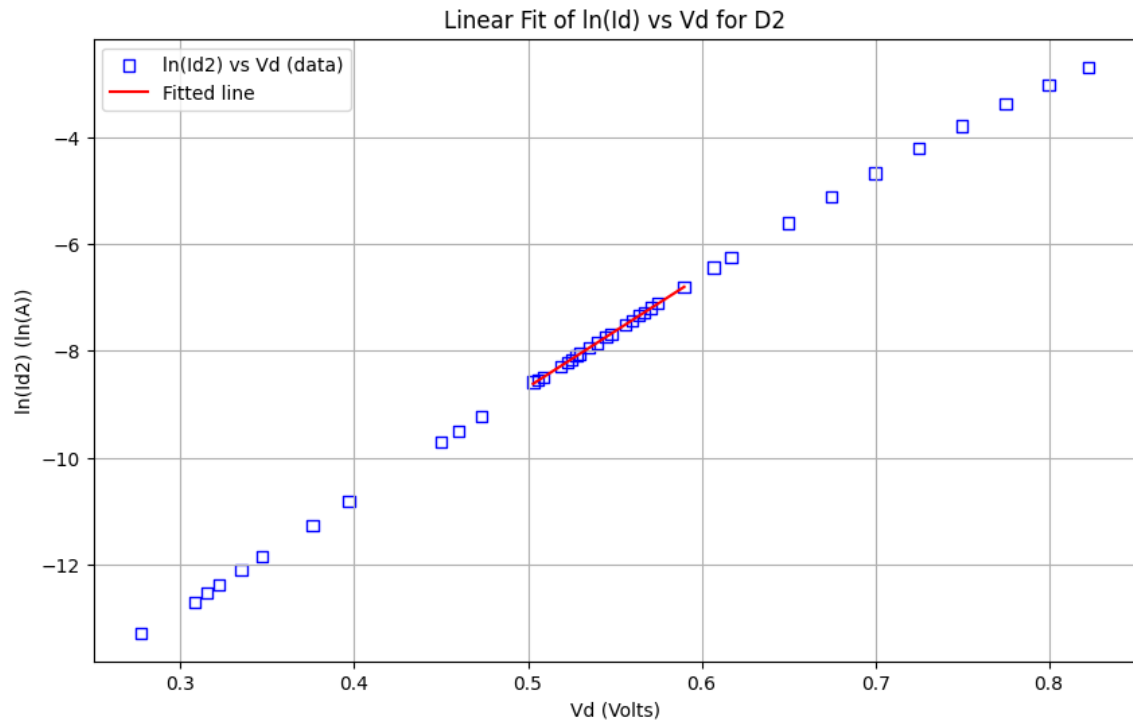


Figure 4: Fitted line on V_D v/s I_D of D2

 


Figure 5: V_{out} of the Log Anti-Log Amplifier

1.4 Conclusion and Inference

1. How to select the diode for log amplification?

- Choose a diode with a linear $\ln(I_D)$ vs V_D relationship over a suitable current range.
- Avoid diodes with multiple linear regions (e.g., D4 in the graph in handout).

2. How to select the input voltage range?

- Determine the range where $\ln(I_D)$ vs V_D is linear.
- Use $V_{in1} = I_{D1}/R$ and $V_{in2} = I_{D2}/R$.

3. How to extract diode model parameters?

- The saturation current I_S is obtained from the y-intercept of the $\ln(I_D)$ vs V_D plot.
- The ideality factor n is extracted from the slope.

4. Which op-amp to choose?

- Choose a low-bias current op-amp like TL084, since high bias currents can distort low-current diode operation.

5. Simulation Steps:

- Plot $\ln(I_D)$ vs V_D for provided diodes.
- Identify the linear range and determine I_S and n .
- Implement the SPICE model for these diodes.
- Verify circuit behavior with expected $\ln(V_{out})$ vs $\ln(V_{in})$.

1.5 Experiment Completion Status

The complete experiment was performed in front of the TA in the lab itself.