
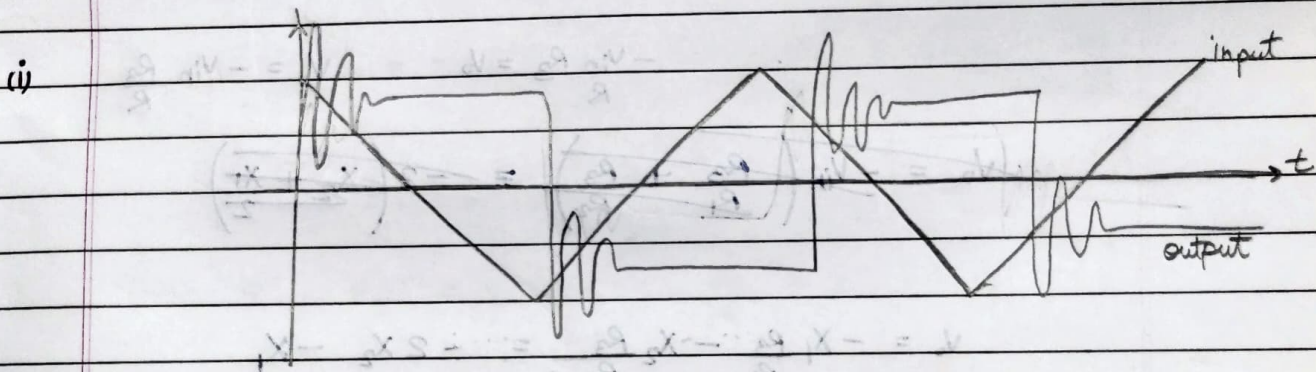



Lab 2

1 OpAmp based Negative feedback circuits

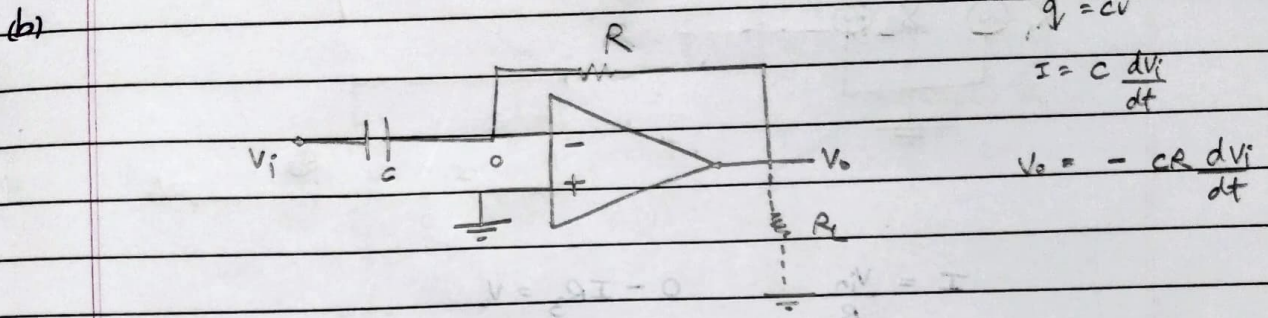(a) After a value of 15V, the amplifier gets saturated.




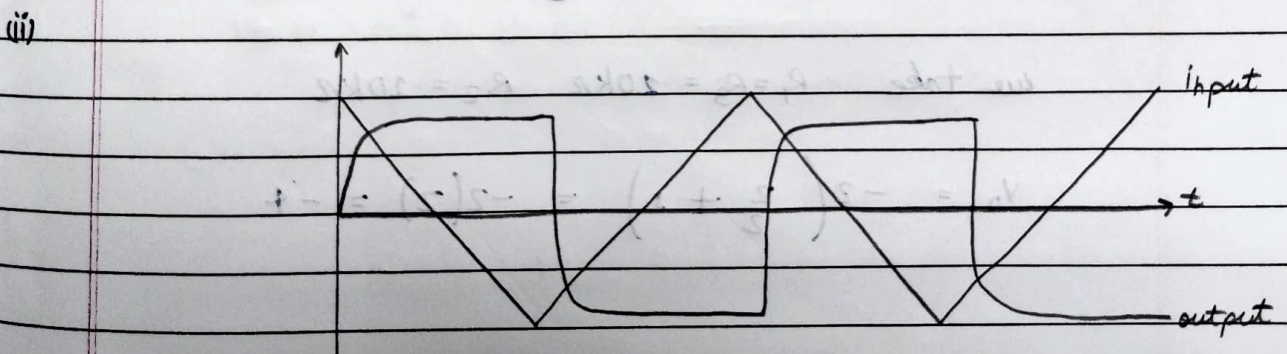(ii) The reason we are getting ripple is Cripp's Phenomenon.



By connecting the capacitor in parallel to the resistor, the output waveform gets smoother out by the capacitor's high frequency filtering effect.

c)

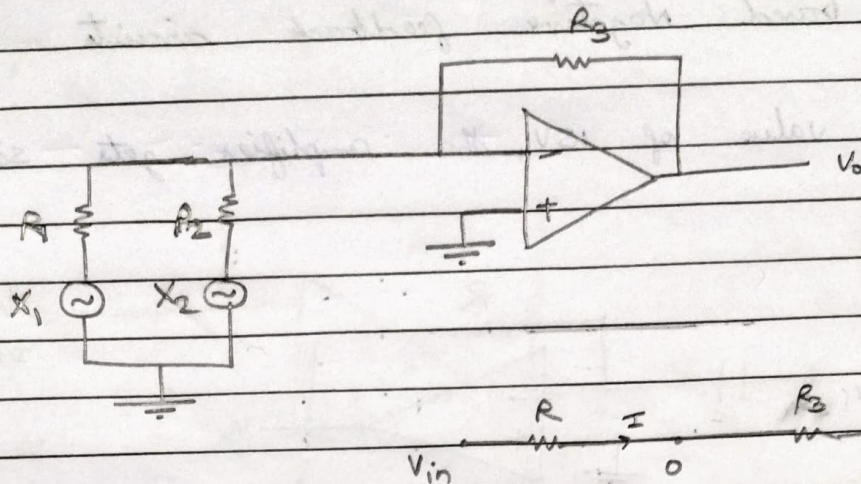

$$I = \frac{V_{in}}{R}$$

$$0 - IR_3 = V_0$$

$$-V_{in} \frac{R_3}{R} = V_0$$

$$V_0 = -V_{in} \frac{R_3}{R}$$

$$V_0 = -V_{in} \left(\frac{R_3}{R_1} + \frac{R_3}{R_2} \right) = -2 \left(\frac{X_2 + \frac{X_1}{2}}{2} \right)$$

$$V_0 = -X_1 \frac{R_3}{R_1} - X_2 \frac{R_3}{R_2} = -2X_2 - X_1$$

$$\frac{R_3}{R_1} = 1 \quad \frac{R_3}{R_2} = 2$$

$$R_1 = R_3 \quad R_2 = \frac{R_3}{2}$$

$$X_1 = V_{pp} \sin$$

$$X_2 = 1V \text{ DC}$$


$$\text{we take } R_1 = R_3 = 20K\Omega \quad R_2 = 10K\Omega$$

$$V_0 = -2 \left(\frac{2}{2} + 1 \right) = -2(2) = -4$$

We are getting V_0 corresponding to the values of X_1 , X_2 , R_1 , R_2 and R_3 .

$$V_o = - \left(0.0001 \frac{d}{dt} X_1 + 2X_2 \right)$$
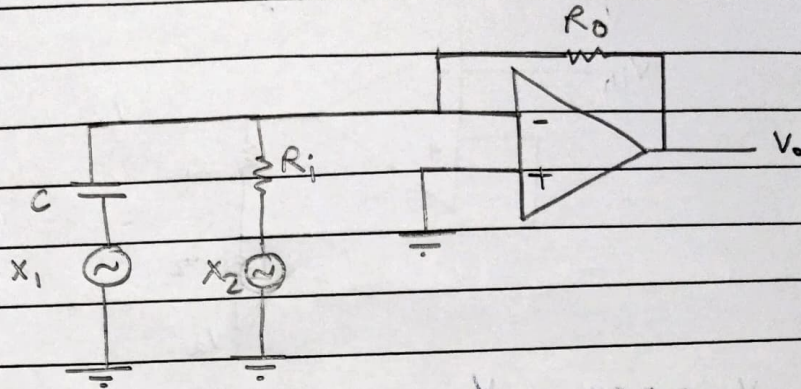
$$V_o = - 0.0001 \frac{d}{dt} X_1 - 2X_2$$



$$V_o = - R_o C \frac{dX_1}{dt} - X_2 \frac{R_o}{R_i} = - 0.0001 \frac{dX_1}{dt} - 2X_2$$

$$\Rightarrow R_o C = 0.0001 \quad \frac{R_o}{R_i} = 2$$


Let $R_i = 5k\Omega$ $R_o = 10k\Omega$ $C = \frac{10^{-4}}{R_o} = \frac{10^{-4}}{10 \times 10^3} = 10^{-8} F$

$$V_{pp} \text{ of output} = 20.2V$$

$$\text{frequency of output} = 500Hz$$

2. Op Amp Based Positive Feedback Circuits

(a) Schmitt Trigger Circuit

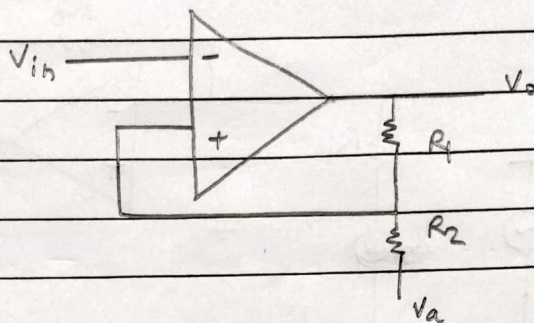

$$V_{TH} = 2.5V \quad V_{TL} = -2.5V \quad V_a = 0$$

$$V_{TH} = V_a + \frac{R_2}{R_1 + R_2} V_{TH \text{ supply}}$$

$$2.5 = 0 + \frac{R_2}{R_1 + R_2} (15)$$

$$\frac{25}{15} = \frac{R_2}{R_1 + R_2} = \frac{1}{6}$$

$$\frac{R_2 + R_1}{R_2} = 6 + 1 = \frac{R_1 + 1}{R_2}$$

$$\Rightarrow \frac{R_1}{R_2} = 5 \quad \Rightarrow R_1 = 5R_2$$

$$\text{let } R_2 = 1k\Omega \quad R_1 = 5k\Omega$$

$$(iii) \quad V_{TH} (\text{measured}) = 2.6V$$

$$V_{TH} (\text{calculated}) = 2.5V$$

(iv)

$$V_{Th} = V_a + \frac{R_2}{R_1 + R_2} V_{supply}$$

$$R_1 = 5K\Omega$$

$$R_2 = 1K\Omega$$

$$= 2 + \frac{1}{6} (15) = 2 + \frac{15}{6} = 2 + \frac{5}{2} = 2 + 2.5 = 4.5V$$

$$V_{TL} = 2 - 2.5V = -0.5V$$


(v)

$$V_{Th} \text{ (measured)} = 4.32V$$

$$V_{Th} \text{ (calculated)} = 4.5V$$

(vi)

(b)

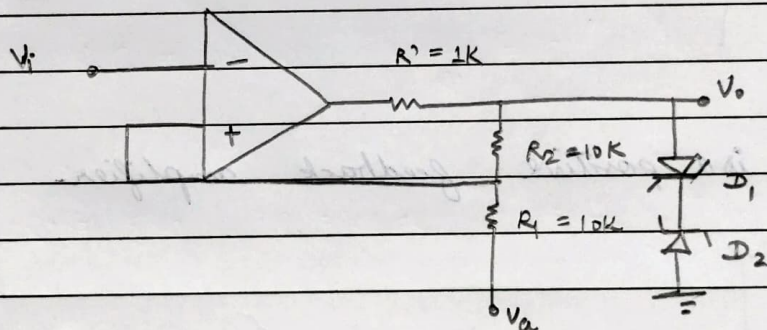

(ii)

R' limits the current through the zener diode when they clamp the circuit.

When R' is removed, a high current might flow, damaging the circuit.

(iv)


$$V_{Th} = V_a +$$

$$V_{Th} \text{ (measured)} = 3.2V$$

$$V_{TL} \text{ (measured)} = -3.2V$$


3. Op Amp Based Feedback Circuit

(i)

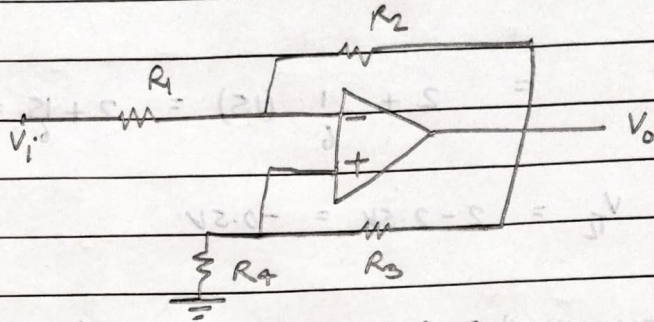

This is a negative feedback amplifier.


(ii)

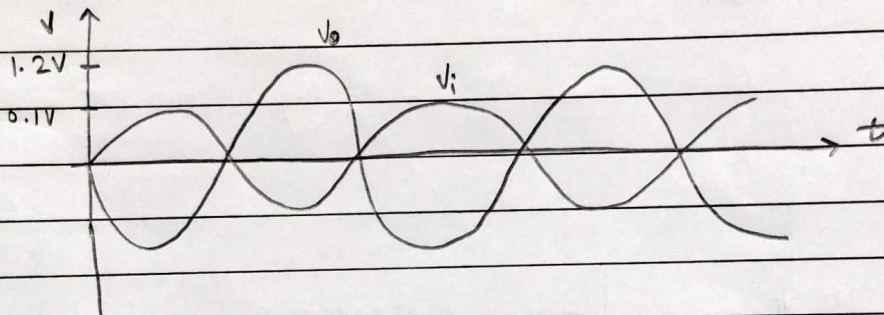

(iii)

This is a positive feedback amplifier.

(iv)

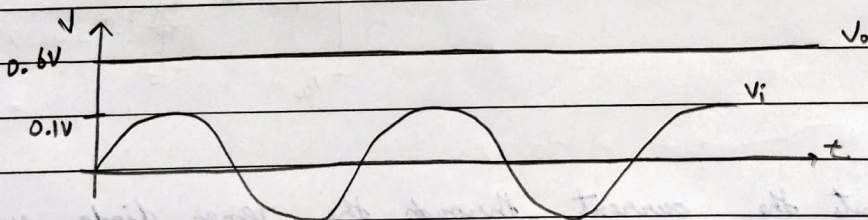

Naman
19/01/25