



Indian Institute of Technology Bombay

**Analog Circuits Lab
EE 230**

**Lab 11 - Electrocardiogram Simulation
April 14, 2025**

**Mridul Choudhary
23B3933**

Contents

1	2nd-Order Low-Pass Filter	2
1.1	Aim	2
1.2	Design	2
1.3	Simulation results	3
1.4	Conclusions	5
2	50Hz Notch Filter	6
2.1	Aim	6
2.2	Design	6
2.3	Simulation results	7
2.4	Conclusions	9
3	Combined Response of LPF + Notch	10
3.1	Aim	10
3.2	Design	10
3.3	Simulation results	11
3.4	Conclusions	11
4	Calculations	12

1 2nd-Order Low-Pass Filter

1.1 Aim

Design and simulate a 2nd-order low-pass ECG amplifier stage that:

1. Provides a DC gain of approximately 28dB
2. Exhibits a 3dB cutoff frequency of 150Hz
3. Uses ideal op-amp assumptions for analytical transfer functions

1.2 Design

1. **Topology:** Two cascaded inverting stages.

2. **Transfer Function:**

$$\frac{V_c}{V_{in}} = -A \times \frac{1}{1 + s\tau_1} \times \frac{1}{1 + s\tau_2} \quad (1)$$

with DC gain A and time constants $\tau_1 = R_7C_2$, $\tau_2 = R_8C_3$.

3. **Component Selection:**

- Adjust resistor ratio to set gain: $A = 10^{(28dB/20)} \approx 25$; so $R_7/R_6 \approx 25$ which gives us $R_7 = 472.256k\Omega$
- And 3dB frequency = 150Hz gives us $R_8 = 361.075k$

4. **Simulation Steps:**

- **AC Sweep (1Hz–10kHz, decade):** Plot magnitude of V_c ; extract DC gain and f_{3dB} .
- **Transient Response (2kHz, $1V_{pp}$):** Observe input vs. output sine waves.

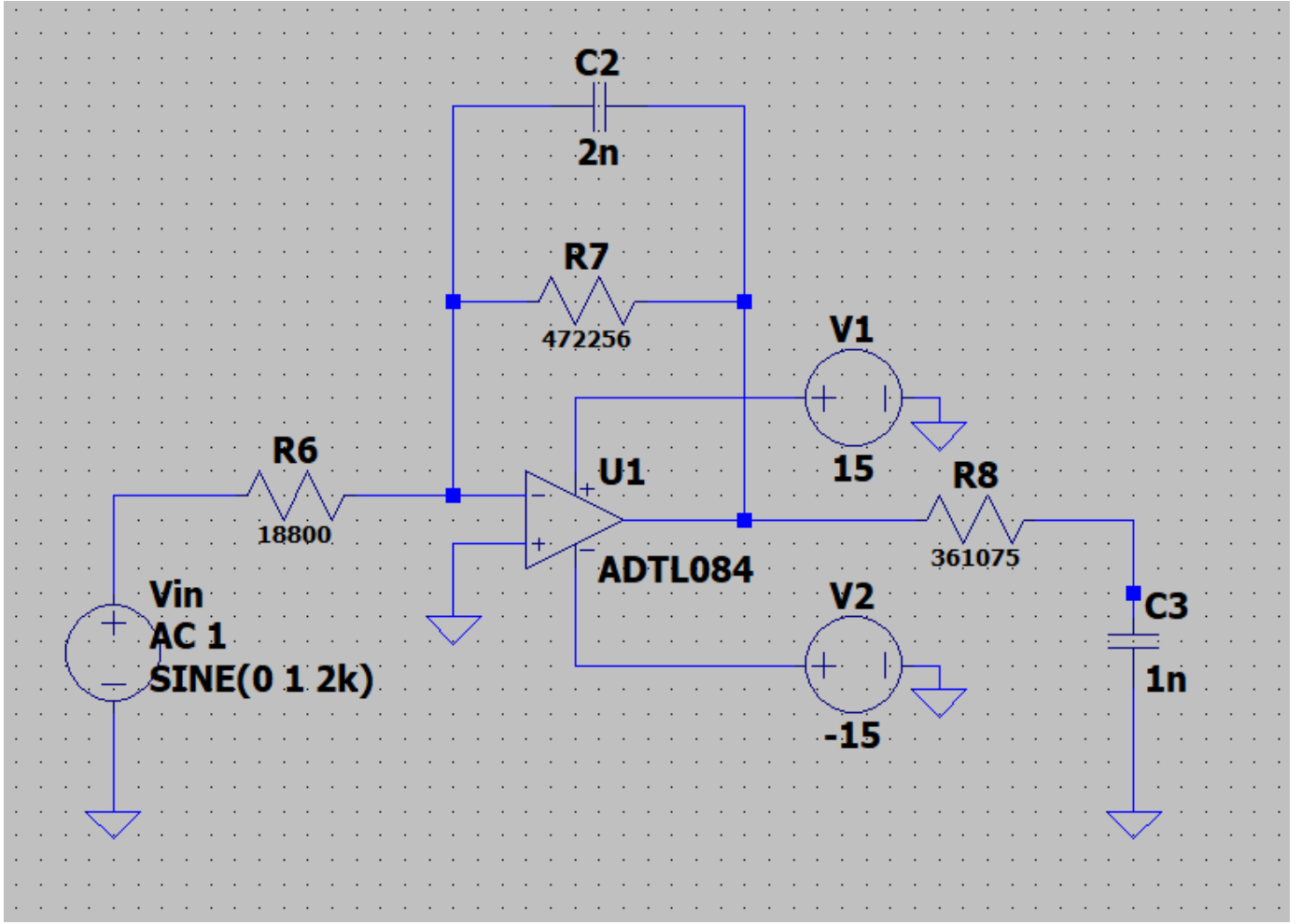


Figure 1: 2nd Order Low Pass Filter

1.3 Simulation results

Sr. No.	Parameter	Value
1	R_6	18.8k Ω
2	R_7	472.256k Ω
3	R_8	361k Ω
4	C_2	2nF
5	C_3	1nF

Table 1: Parameter Values

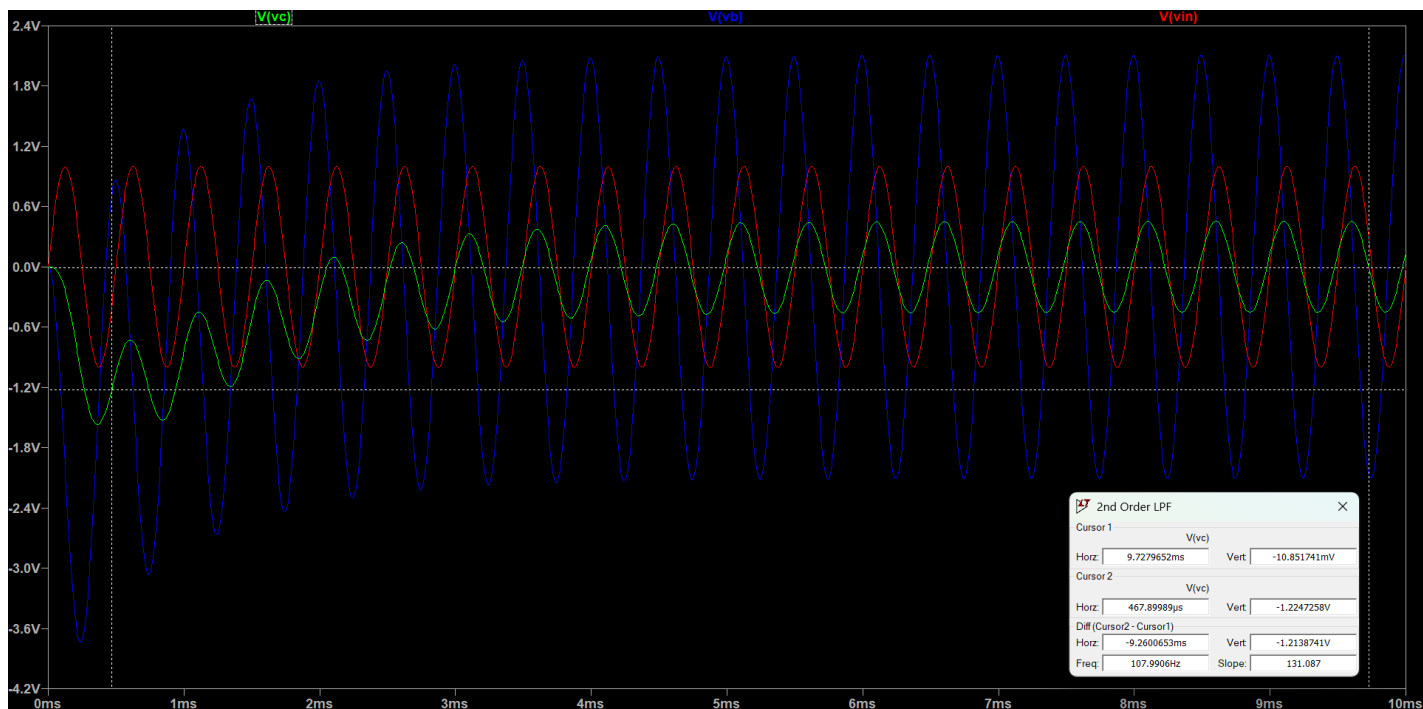


Figure 2: AC Analysis

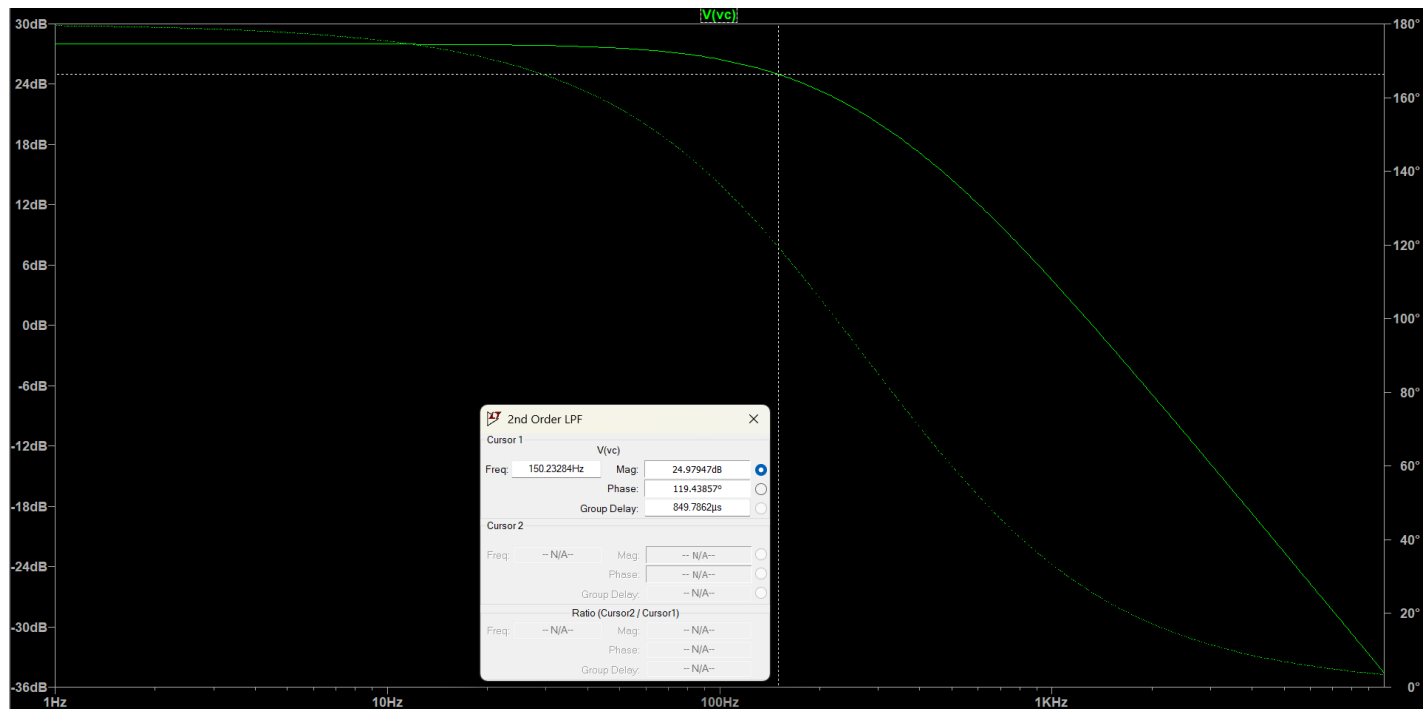


Figure 3: Transient Analysis

1.4 Conclusions

1. **DC Gain:** $\sim 28\text{dB}$ (measured)
2. **3dB Cutoff:** $\sim 150\text{Hz}$
3. **Transient Behavior:** Attenuation of high-frequency components; clean sine at output with expected amplitude scaling.

Thus, the designed filter meets the specifications, providing the desired gain and cutoff, and behaves as a stable 2nd-order low-pass stage.

2 50Hz Notch Filter

2.1 Aim

Implement and simulate a twin-T notch filter that suppresses 50Hz interference by combining:

1. A **low-pass section** (cutoff 20–30Hz)
2. A **high-pass section** (cutoff 80–90Hz)
3. **Summing network to notch at 50Hz**

2.2 Design

1. Low-Pass Filter (LPF):

- Single-pole RC: $f_{c,LP} = \frac{1}{2\pi R_9 C_6} \rightarrow$ choose R_9 for 25Hz cutoff.
- With $C_6 = 220nF$, we get $R_9 = 28.397k\Omega$.
- **AC Analysis (1Hz–1kHz):** Plot voltage across C_6 .

2. High-Pass Section (HPF):

- Single-pole RC: $f_{c,HP} = \frac{1}{2\pi R_{10} C_4} \rightarrow$ choose R_9 for 85Hz cutoff.
- With $C_4 = 100nF$, we get $R_{10} = 18.724k\Omega$.
- **AC Analysis (0.1Hz–1kHz):** Plot voltage across R_{10} .

3. Notch Network:

- Combine LPF output and inverted HPF output (twin-T topology).
- **AC Analysis (0.1Hz–1kHz):** Plot V_{out} ; tabulate notch depth and half-power frequencies around notch.

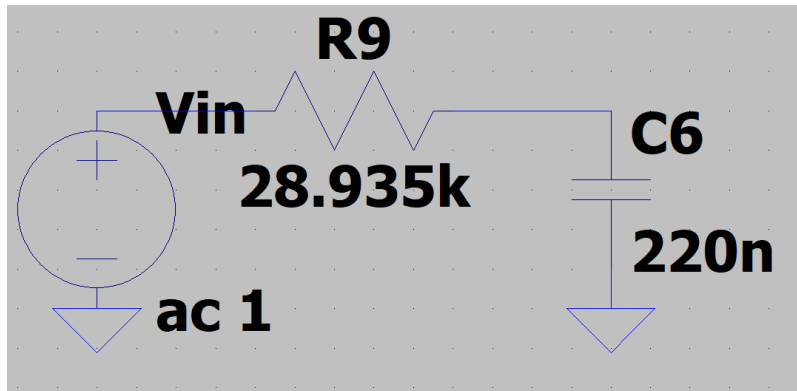


Figure 4: The Low-Pass Filter

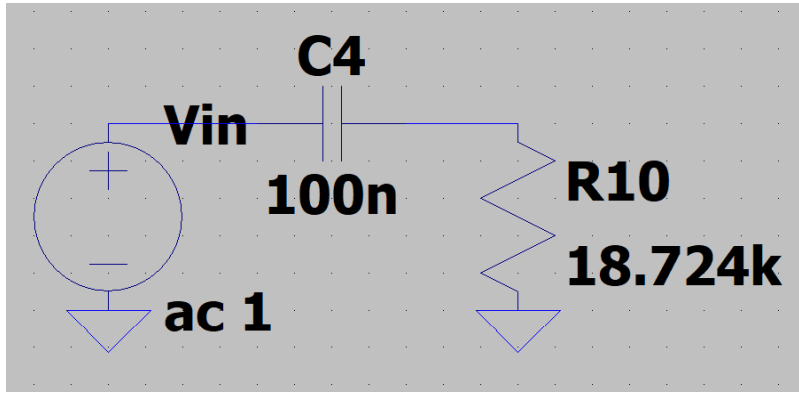


Figure 5: The High-Pass Filter

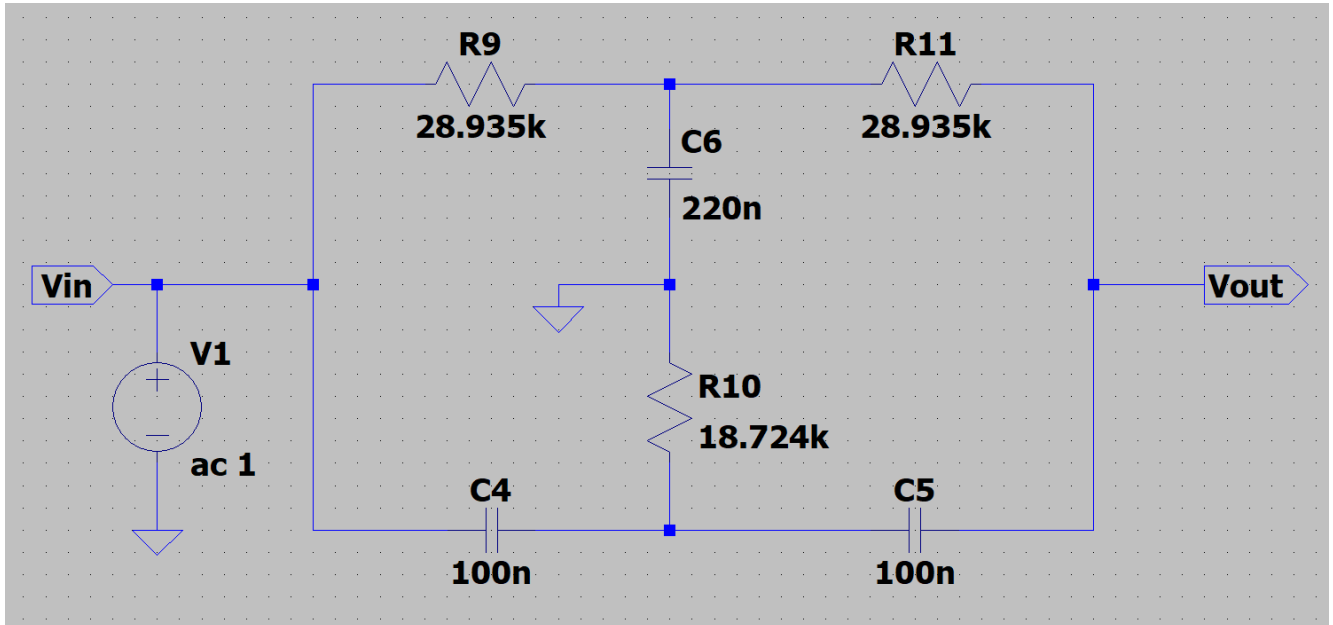


Figure 6: The High-Pass Filter

2.3 Simulation results

Sr. No.	Parameter	Value
1	R_9	$28.935\text{k}\Omega$
2	C_6	220nF
3	R_{10}	$18.724\text{k}\Omega$
4	C_4	100nF

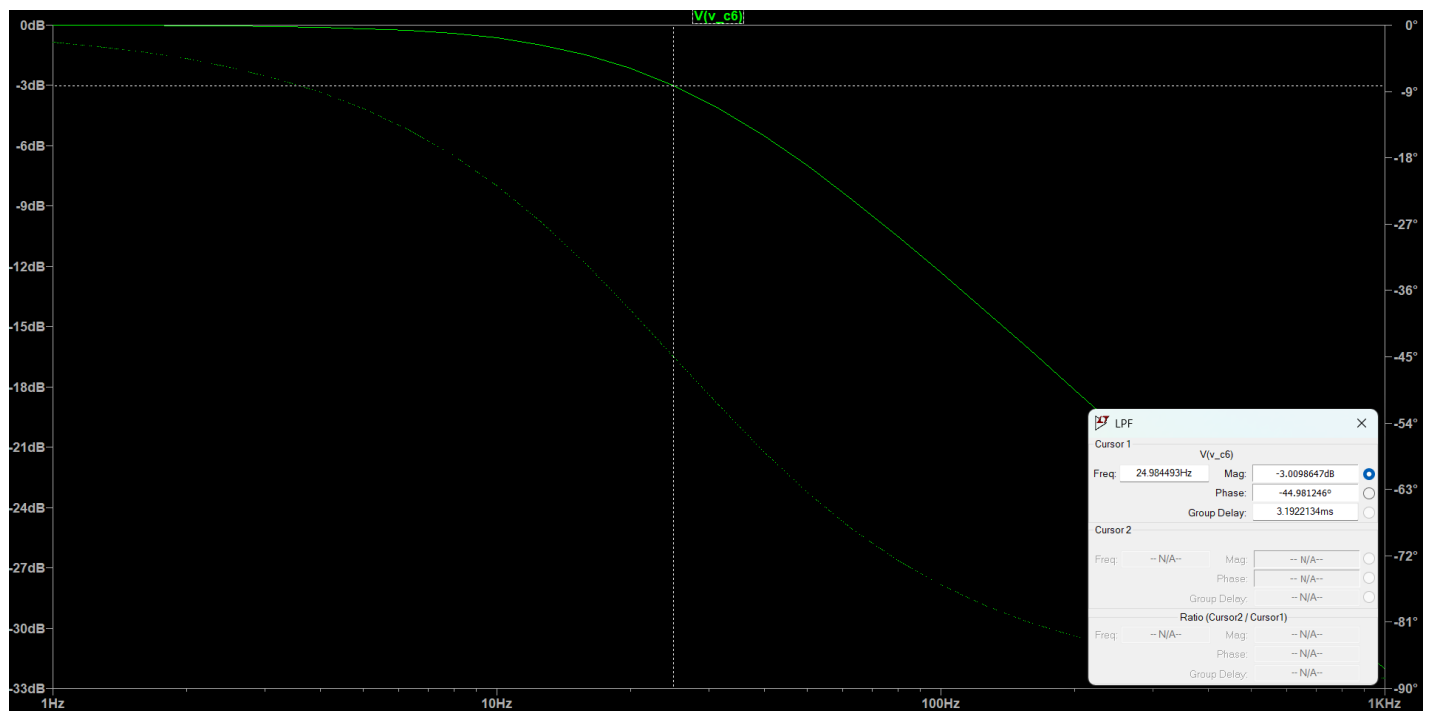


Figure 7: The Low-Pass Filter Characteristics

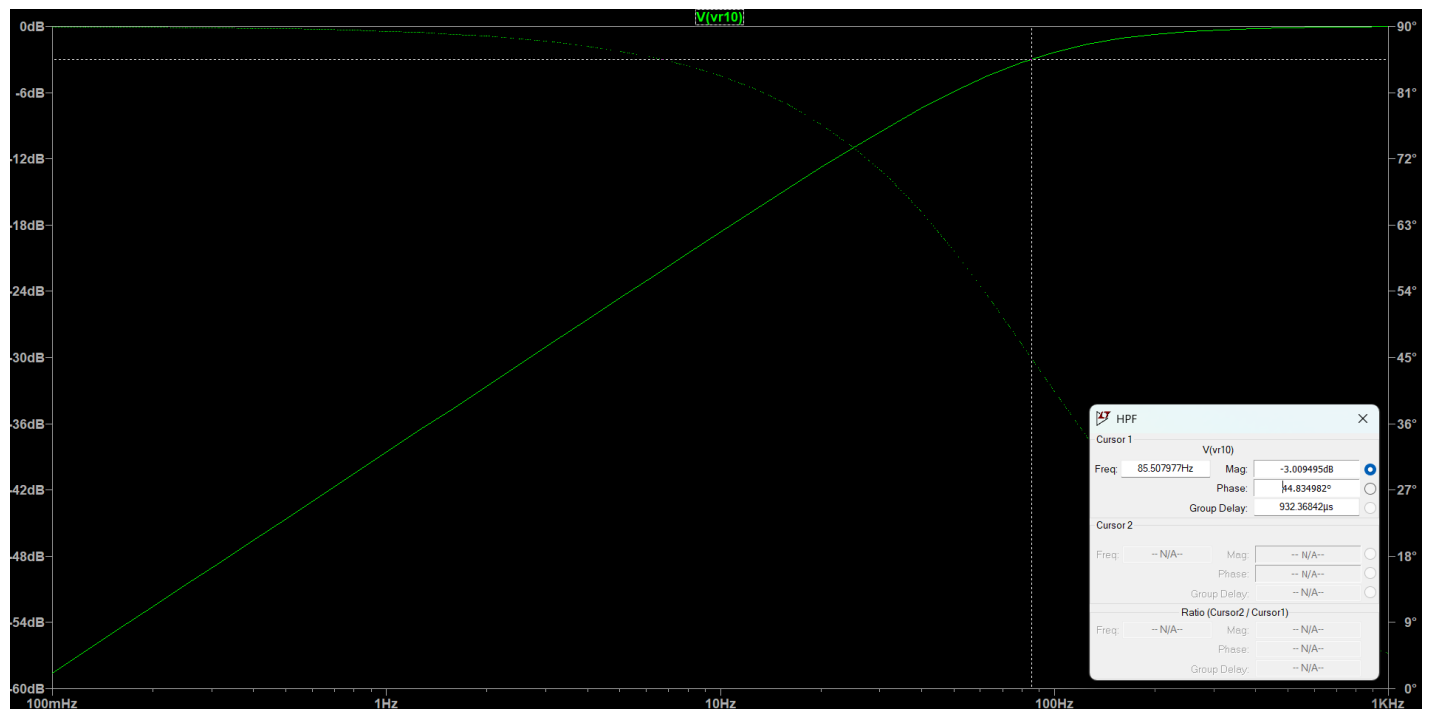


Figure 8: The High-Pass Filter Characteristics

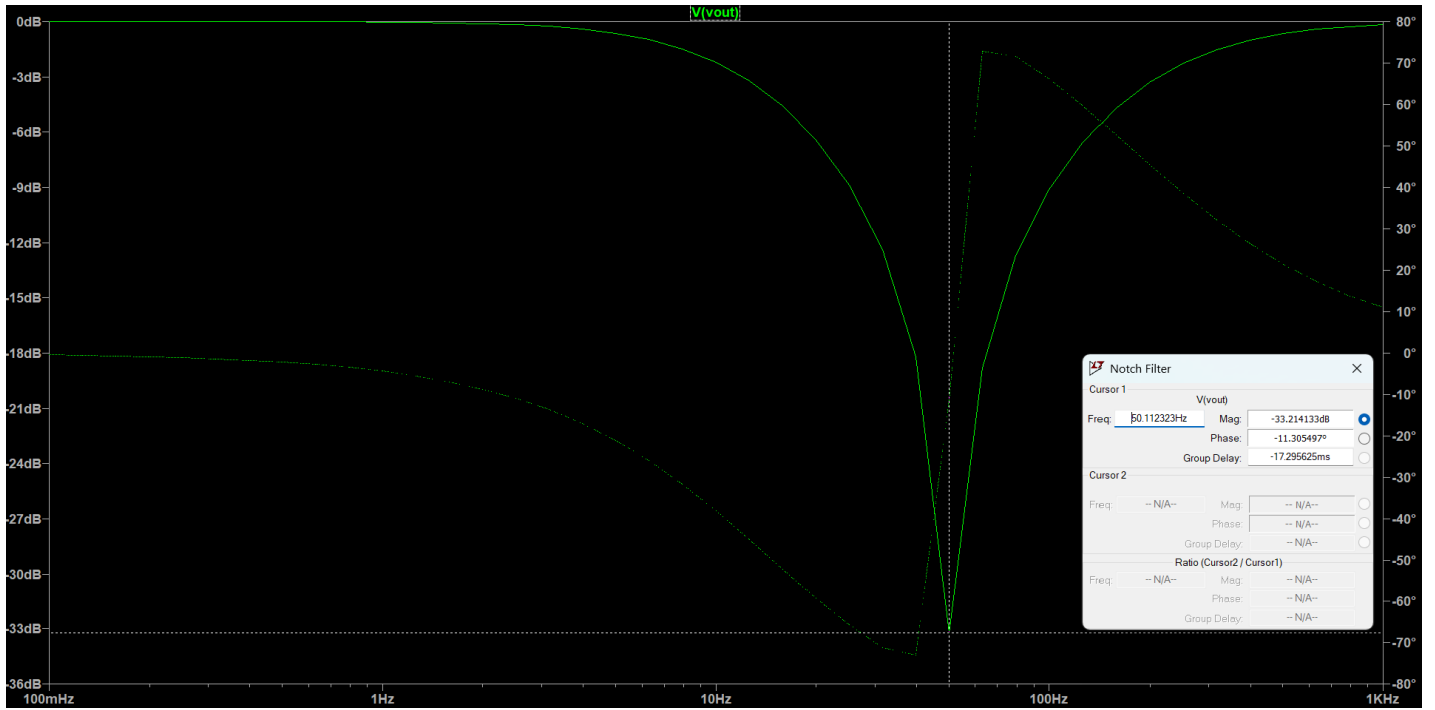


Figure 9: The Notch Characteristics

2.4 Conclusions

1. **LPF Cutoff:** 24.98Hz \sim 25Hz
2. **HPF Cutoff:** 85.5Hz \sim 85Hz
3. **Notch Depth:** 30dB attenuation at 50Hz
4. **Bandwidth Around Notch:** $\sim \pm 5$ Hz

The twin-T network effectively rejects 50Hz interference while passing frequencies outside the notch with minimal distortion.

3 Combined Response of LPF + Notch

3.1 Aim

Integrate the 2nd-order low-pass filter (Part (a)) with the 50Hz notch filter (Part (b)) and characterize the overall ECG amplifier response:

1. Measure DC gain and overall 3dB cutoff
2. Verify transient responses at representative frequencies (20Hz, 50Hz, 100Hz, 2kHz)

3.2 Design

1. **Topology:** Cascade of Part(a) filter into Part(b) notch network.
2. **AC Analysis (0.1Hz–1kHz):**
 - Plot combined V_{out}
 - Extract overall DC gain ($\sim 28\text{dB}$) and 3dB cutoff ($\sim 150\text{Hz}$).
3. **Transient Simulations:**
 - **20Hz:** Low-frequency ECG component passes with correct gain.
 - **50Hz:** Notch yields deep attenuation in time-domain.
 - **100Hz & 2kHz:** Observe roll-off per low-pass behavior; high-frequency suppression.

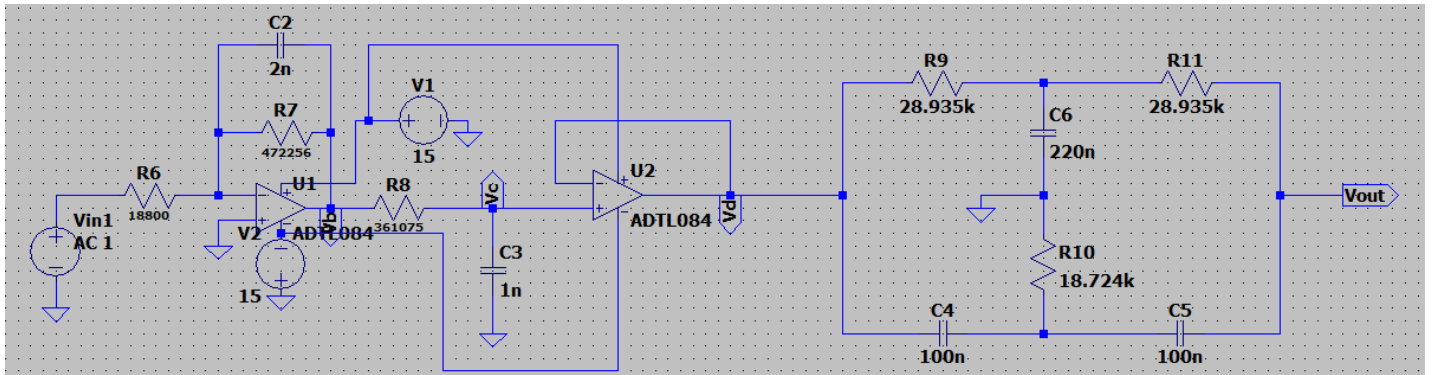


Figure 10: The Combined Circuit

3.3 Simulation results

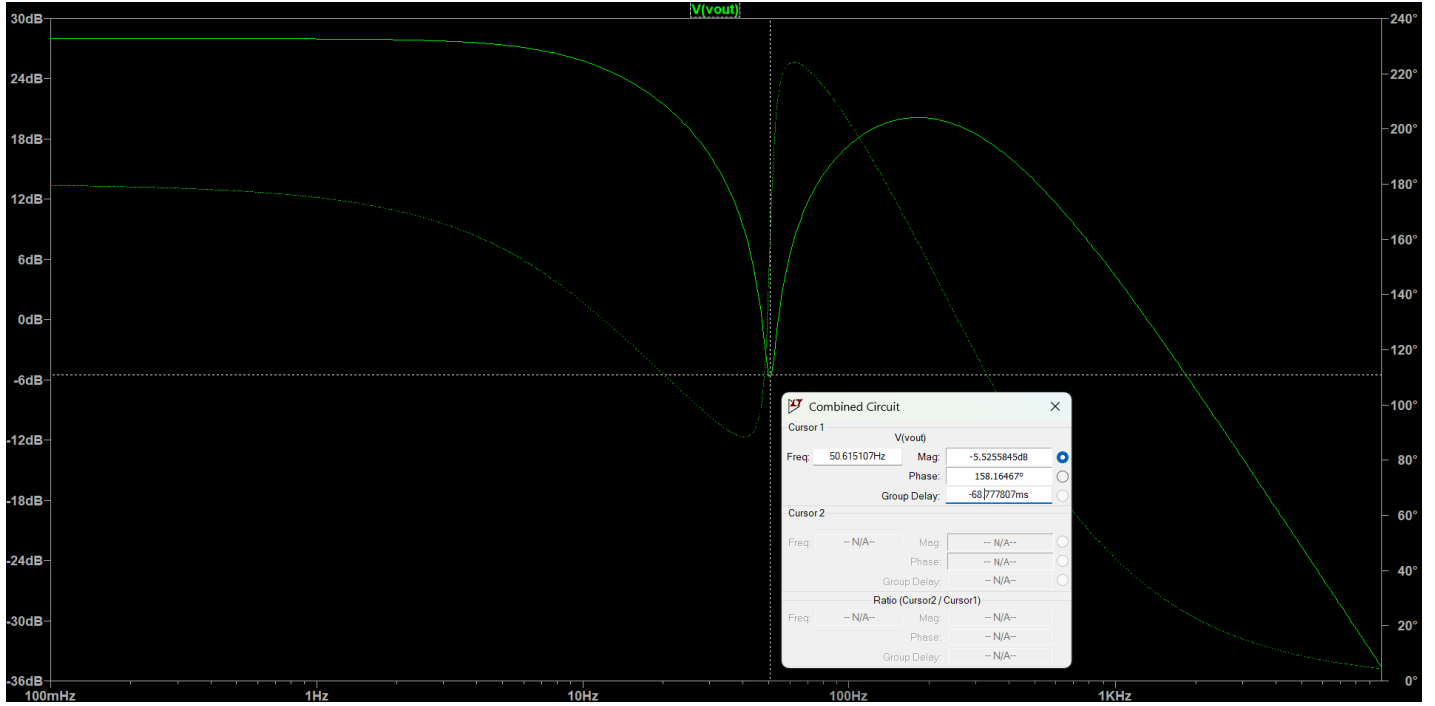


Figure 11: The Combined Circuit Characteristics

3.4 Conclusions

1. **Overall DC Gain:** $\sim 28\text{dB}$
2. **Overall 6dB Cutoff:** $\sim 150\text{Hz}$
3. **Transient Observations:**

- **20 Hz:** Clean amplification. **50 Hz:** Nearly zero output (notch action) **100 Hz & 2 kHz:** Progressive attenuation per filter roll-off.

The combined amplifier meets ECG signal requirements: high gain in passband (0.5–150Hz), strong 50Hz rejection, and suppression of unwanted high-frequency noise.

4 Calculations

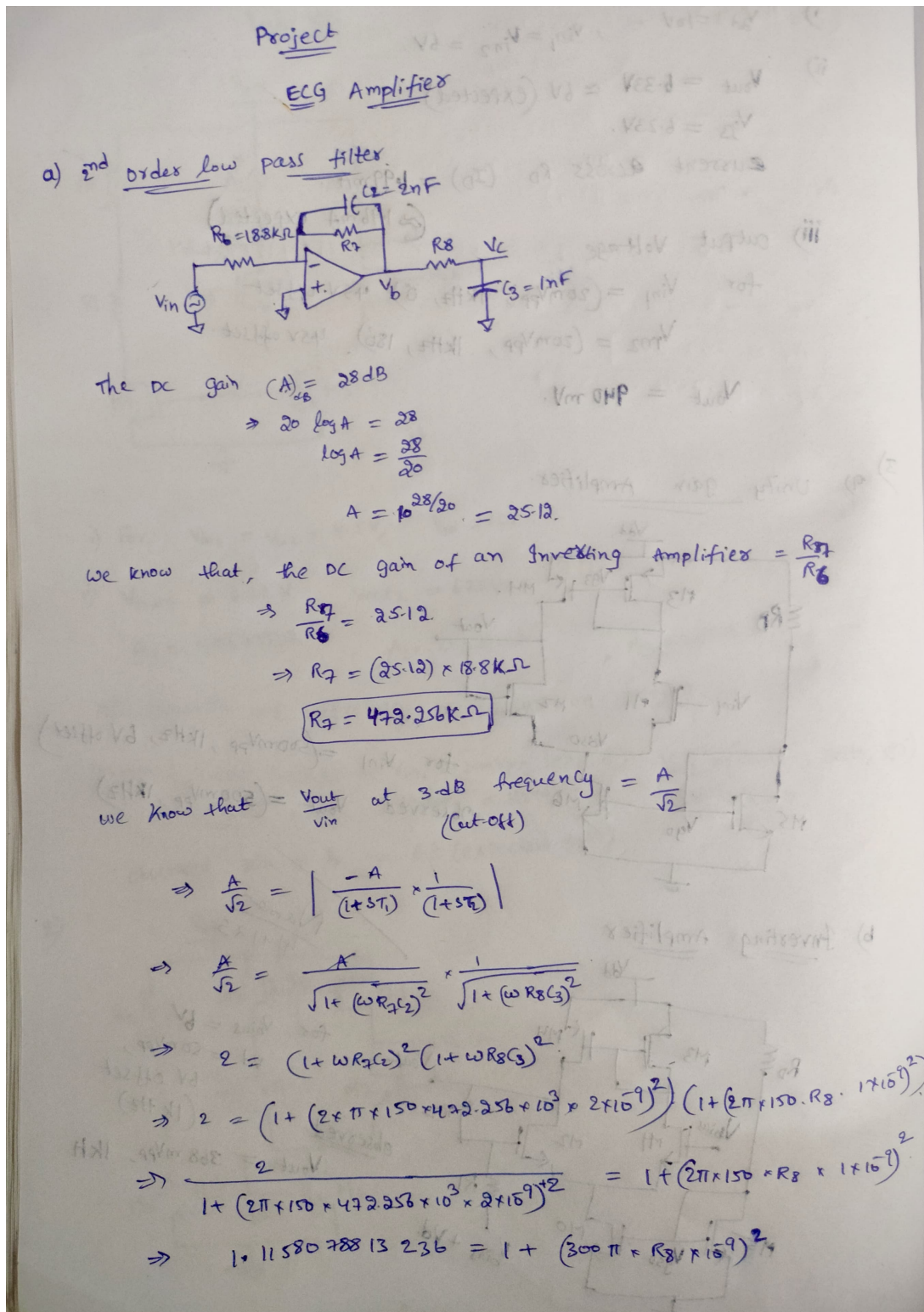


Figure 12: Calculations 1



$$\Rightarrow 0.1158078813236 = (300\pi R_8 \times 10^{-9})^2$$

$$\Rightarrow 0.3403055705151 = 300\pi \times R_8 \times 10^{-9}$$

$$\Rightarrow R_8 = 361075.42472291$$

$$R_8 = 361.075 \text{ k}\Omega$$

b)

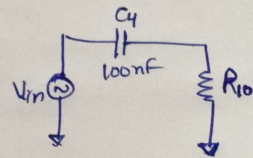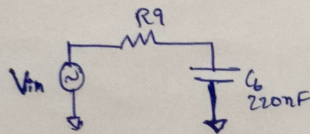

low pass filter
Cut-off frequency $\approx 25 \text{ Hz}$


$$\frac{1}{2\pi C_6 R_9} = 25 \text{ Hz}$$

$$\Rightarrow \frac{1}{2\pi (220 \times 10^{-9}) R_9} = 25$$

$$\Rightarrow R_9 = \frac{1}{2\pi (220 \times 10^{-9}) \times 25}$$

$$R_9 = 28937.26$$

$$R_9 = 28.937 \text{ k}\Omega$$

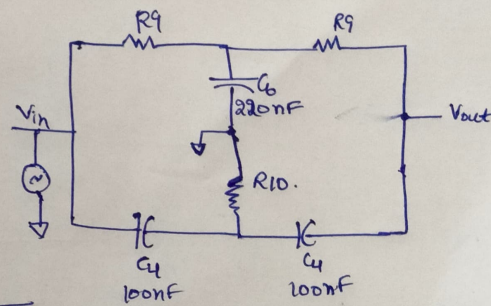

Notch filter $\Rightarrow (50 \text{ Hz})$

High pass filter
Cut-off frequency $\approx 85 \text{ Hz}$

$$\frac{1}{2\pi C_4 (R_{10})} = 85$$

$$\Rightarrow \frac{1}{2\pi (100 \times 10^{-9}) R_{10}} = 85$$

$$\Rightarrow \frac{1}{200\pi \times R_{10} \times 10^{-9}} = 85$$

$$\Rightarrow \frac{10^9}{200\pi \times 85} = R_{10}$$

$$\Rightarrow R_{10} = 18724.11 \Omega = 18.724 \text{ k}\Omega$$

Figure 13: Calculations 2